
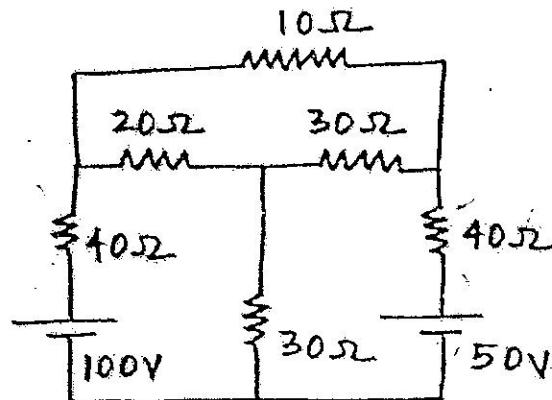


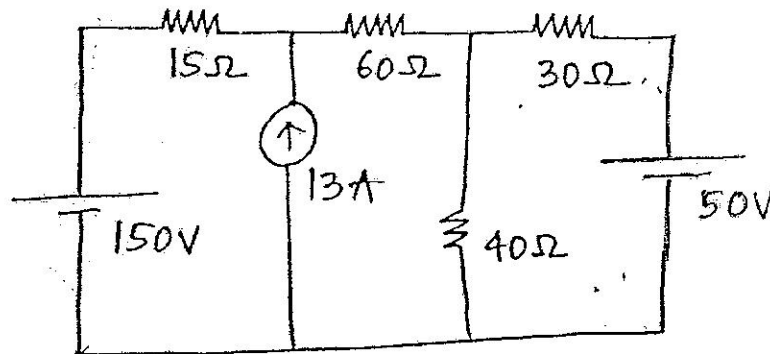1. Find the current through  $10\Omega$  resistor by using Thevenin's Theorem. (May 18) (8 m).




Ans.  $I_{10\Omega} = 0.3798A (\rightarrow)$ .

2. Find the current through  $30\Omega$  resistor by using Thevenin's Theorem. (May 16) (2 m)




Ans.  $I_{30\Omega} = 1.248A (\rightarrow)$ .

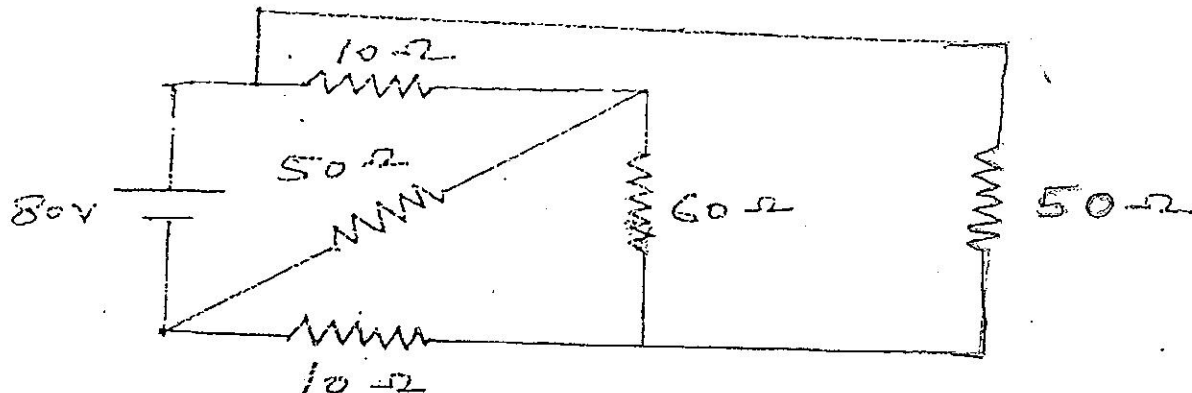3. Find the current through  $60\Omega$  resistor by using Thevenin's Theorem. (May 14) (8 m)




Ans.  $I_{60\Omega} = 0.7A (\downarrow)$ .

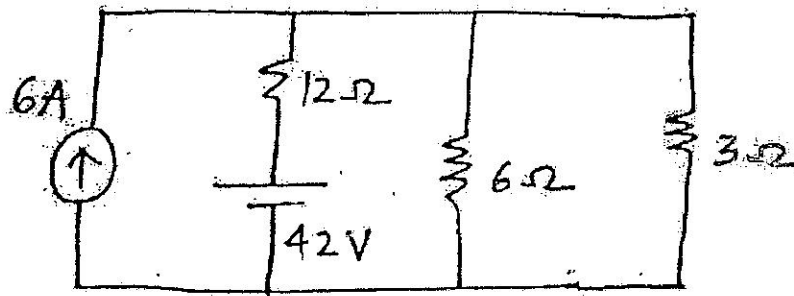4. Find the current through  $3\Omega$  resistor by using Thevenin's Theorem. (May 19) (8 m).




Ans.  $I_{3\Omega} = 5.43A(\downarrow)$ .

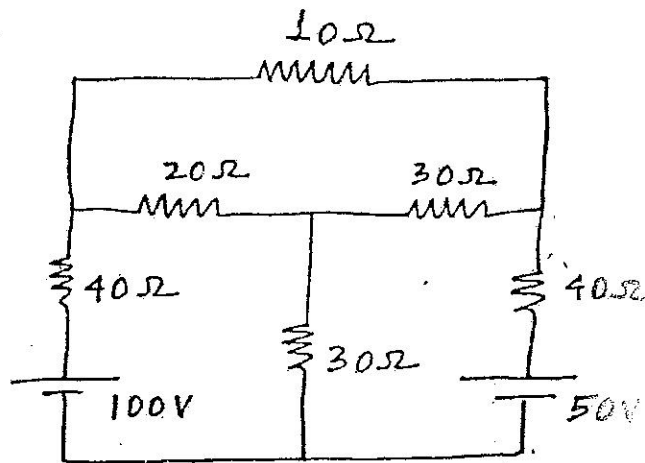5. Find the current through  $10\Omega$  resistor by using Thevenin's Theorem. (May 18) (8 m).




Ans.  $I_{10\Omega} = 0.38A$ .

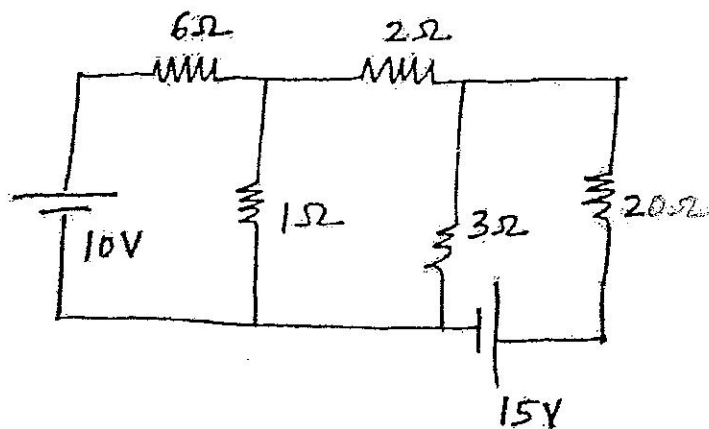6. Find the current through  $20\Omega$  resistor by using Thevenin's Theorem. (May 11) (8 m).




Ans.  $I_{20\Omega} = 0.665A$ .

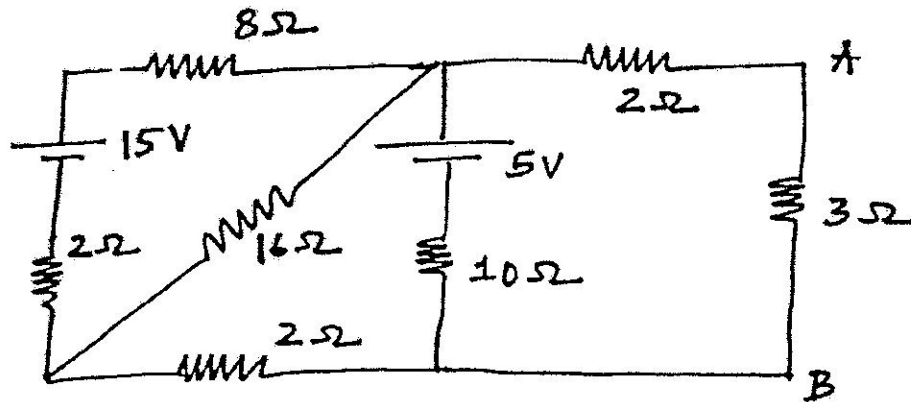7. Obtain Norton equivalent circuit of the network across  $A$  and  $B$ . (Dec 16)(10 m).




Ans.  $I_N = 1.129A$ ,  $R_N = 6.49\Omega$

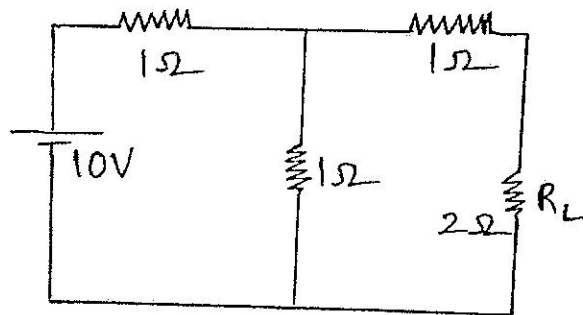8. For the given circuit, find the Norton equivalent between points  $A$  and  $B$ . (May 15)(3 m).




Ans.  $R_N = 1.5\Omega$ ,  $I_N = 3.333A$

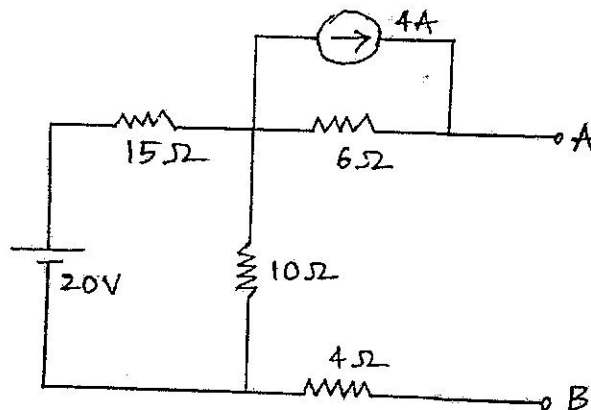9. Find the Norton's equivalent for the linear Network shown:




Ans.  $I = 2A$ ,  $R_N = 16\Omega$ .

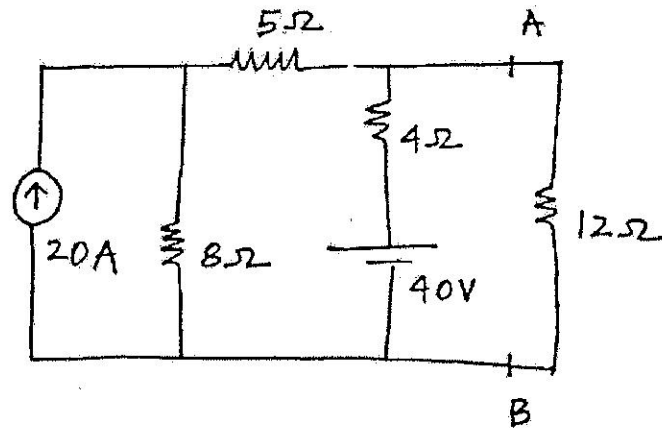10. Find the current through  $12\Omega$  resistor by using Norton's Theorem. (May 17) (8 m).




Ans.  $I_{12\Omega} = 4.53A$ .

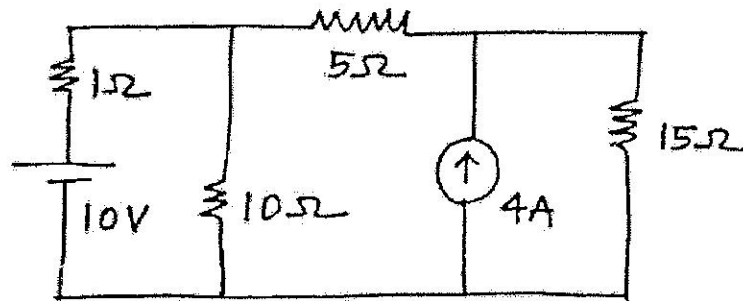11. Find the current through  $10\Omega$  resistor by using Norton's Theorem. (May 17) (8 m).




Ans.  $I_{10\Omega} = 1.130A$ .

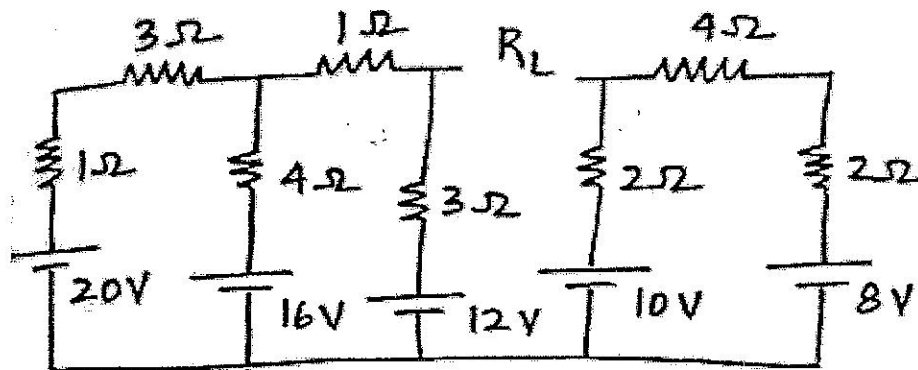12. Find the Magnitude of  $R_L$  which absorbs Maximum Power. Also find magnitude of Maximum Power. (May 18) (8 m).




Ans.  $R_L = 3\Omega$ ,  $P_{L_{max}} = 5.042W$ .

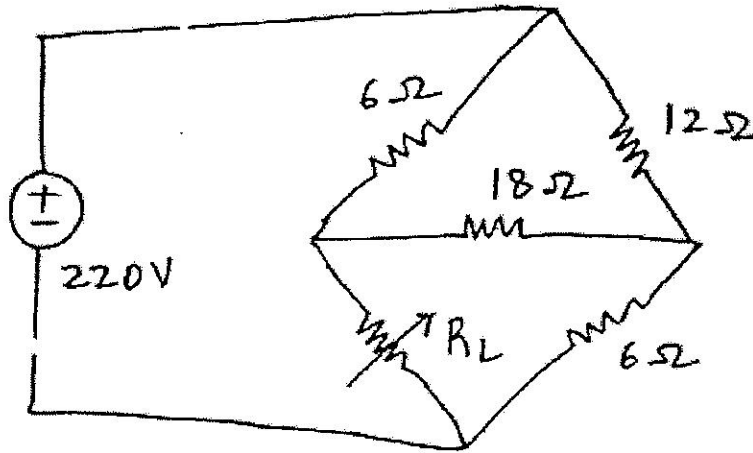13. Find the Magnitude of  $R_L$  which absorbs Maximum Power. Also find magnitude of Maximum Power. (Dec 17) (10 m).




Ans.  $R_L = 4.71\Omega$ ,  $P_{L_{max}} = 1884W$ .

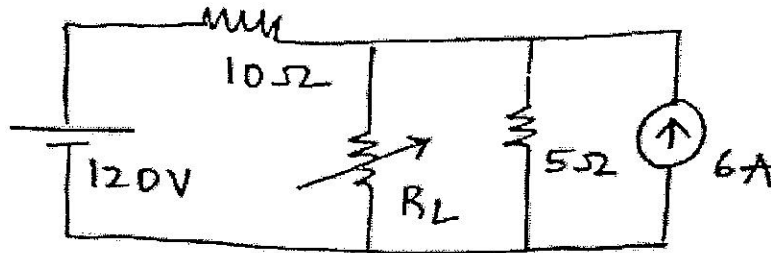14. Find the Magnitude of  $R_L$  which absorbs Maximum Power. Also find magnitude of Maximum Power. (Dec 17) (8 m).




Ans.  $R_L = 3.333\Omega$ ,  $P_{L_{max}} = 270W$ .

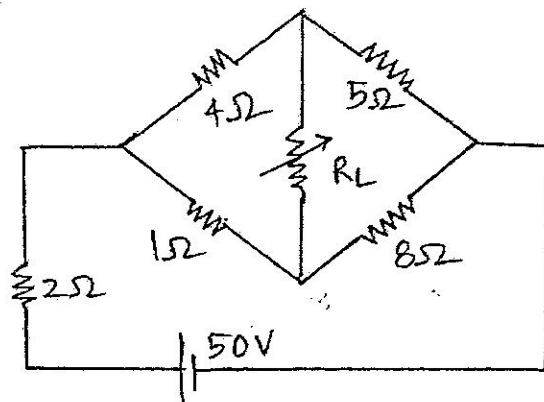15. Find  $R_L$  and  $P_{L_{max}}$ . (Dec 14, May 17) (8 m).




Ans.  $R_L = 3.258\Omega$ ,  $P_{L_{max}} = 10.18W$ .

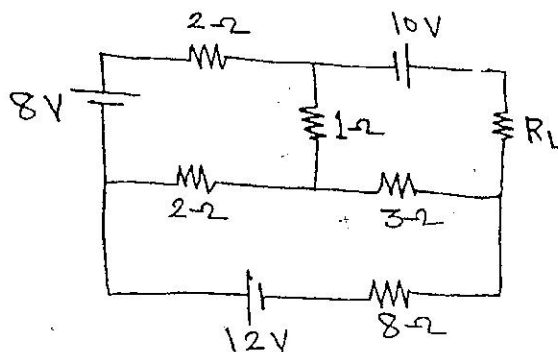16. For the given circuit, find the value of  $R_L$  so the maximum power dissipates in it. Find  $P_{L_{max}}$ . (Dec 13)(8 m).




Ans.  $R_L = 7.6\Omega$ ,  $P_{L_{max}} = 21.974W$ .

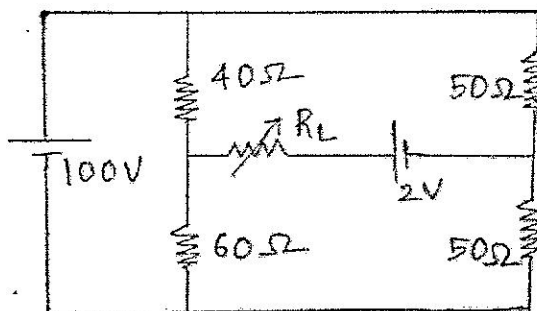17. Find the Magnitude of  $R_L$  which absorbs Maximum Power. Also find magnitude of Maximum Power. (Dec 12)(8 m).



Ans.  $R_L = 24\Omega$ ,  $P_{L_{max}} = 0.326W$ .

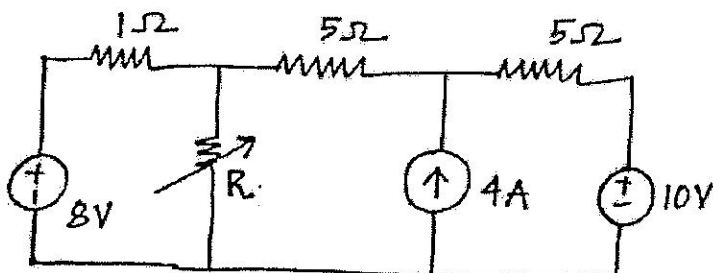18. Find the Magnitude of  $R_L$  which absorbs Maximum Power. Also find magnitude of Maximum Power. (Dec 17)(10 m).



Ans.  $R_L = 0.91\Omega$ ,  $P_{L_{max}} = 27.47W$ .