
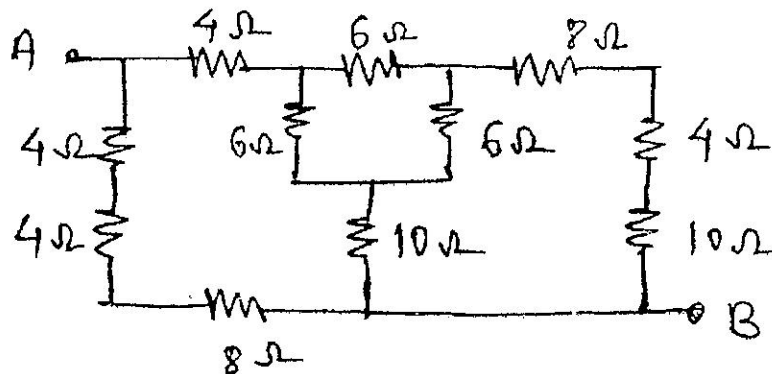


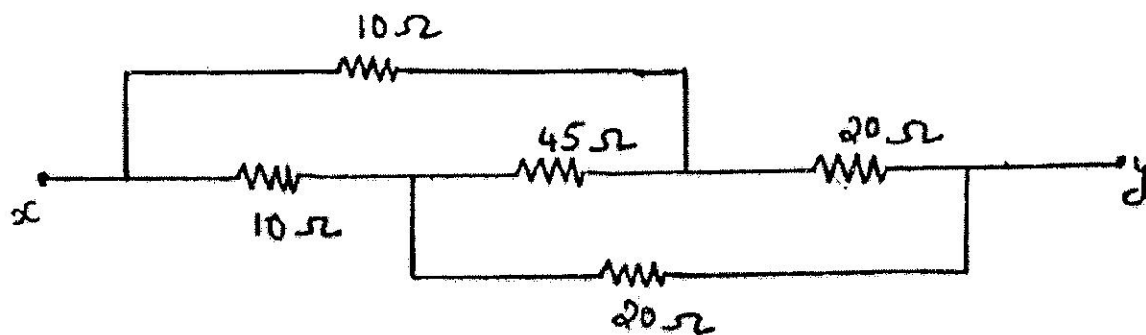1. For the circuit shown below find the resistances between terminals A and B.  
(May 13)(7 m)




Ans.  $R_{AB} = 7.467\Omega$ .

2. Calculate  $R_{xy}$  for the circuit shown in the figure. (Dec 12)(7 m)




Ans.  $R = 15\Omega$ .

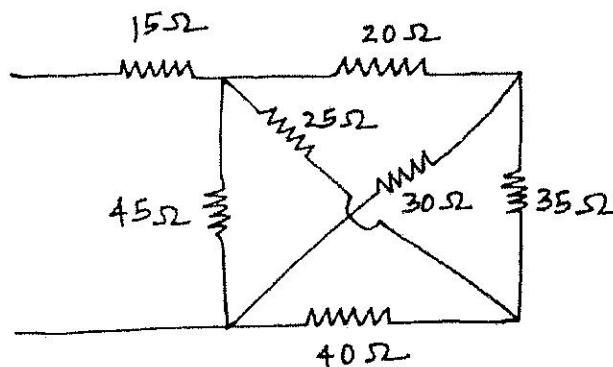3. Find an equivalent resistances between terminals A and B. (May 14)(7 m)




Ans.  $R_{AB} = 32.353\Omega$ .

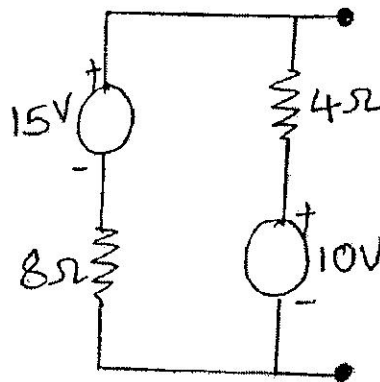7. Using source transformation convert the circuit given below to a single voltage source in series with a resistor. (Dec 12)(7 m)




Ans.  $V = 11.67V$  and  $R = 2.667\Omega$ .

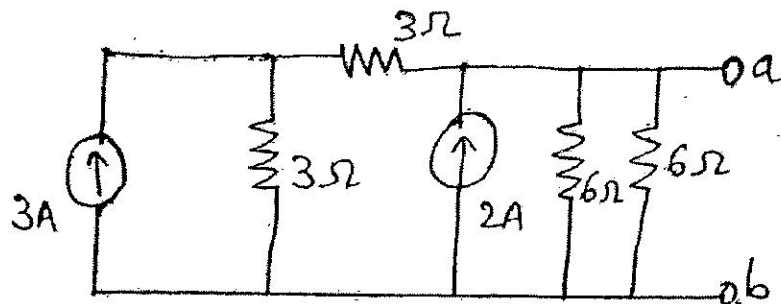8. Using source transformation convert the circuit given below to a single current source in parallel with a resistor. (May 14)(3 m)




Ans.  $I = 3.5A(\uparrow)$  and  $R = 2\Omega$ .

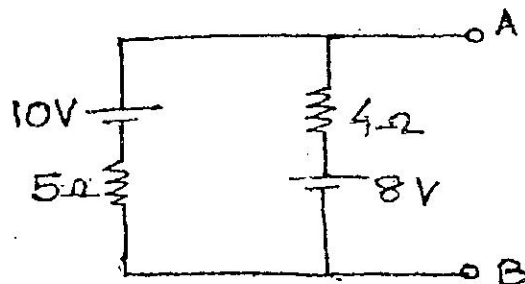9. Convert the given circuit into a current source in parallel with a single resistance between points A and B. (May 13)(3 m)




Ans.  $I = 4A(\uparrow)$ ,  $R = 2.222\Omega$ .

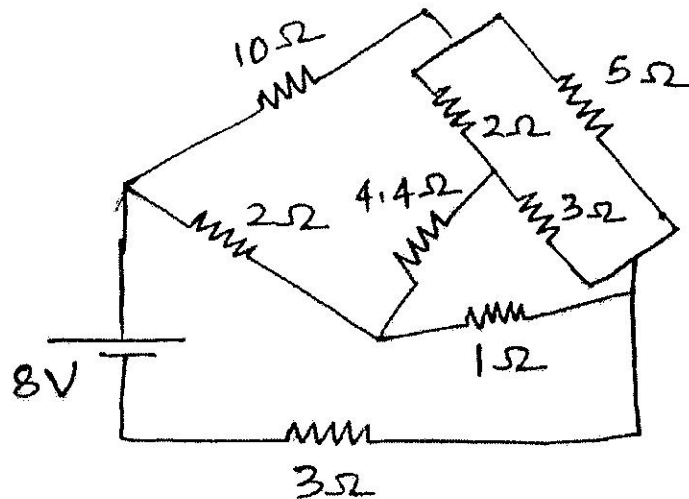4. Find the current delivered by the source. (May 17)(8 m)




Ans.  $I = 1.4864A$ .

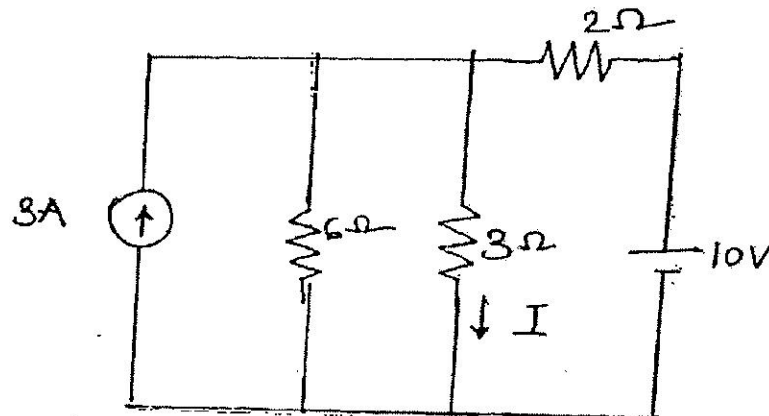5. Using Source Transformation, find  $I$ . (May 11)(5 m)




Ans.  $I = 2.667A(\downarrow)$ .

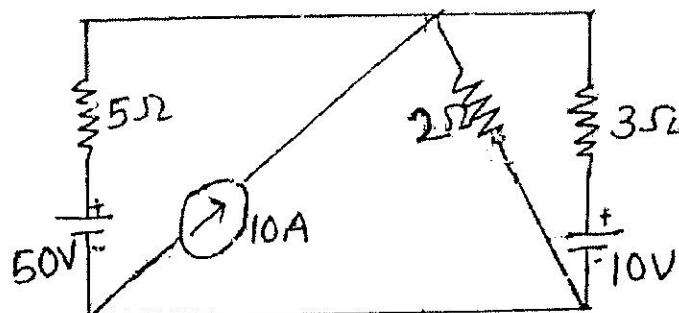6. Find the current through  $5\Omega$  resistor by source transformation. (Dec 12)(3 m)




Ans.  $I_{5\Omega} = 5.484A(\uparrow)$ .

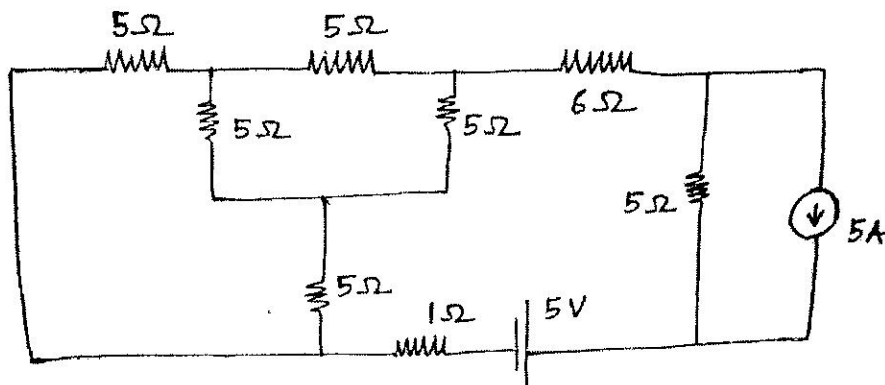10. Using source transformation find the current flowing through the  $6\Omega$  resistance.  
(May 15)(7 m)




Ans.  $I_{6\Omega} = 1.1765A(\rightarrow)$ .

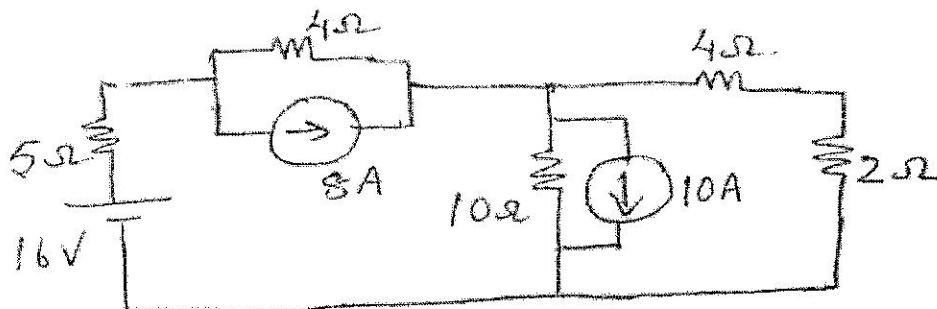11. Using source transformation find the current flowing through the  $2\Omega$  resistance.  
(May 17)(7 m)



Ans.  $I_{2\Omega} = 2.058A(\uparrow)$ .

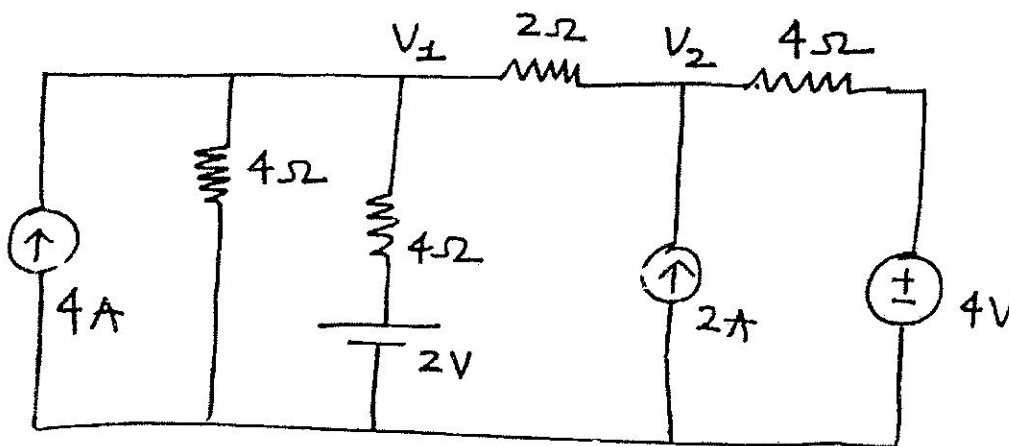12. Using source transformation find  $V_1$  and  $V_2$ .  
(May 18)(7 m)



Ans.  $V_1 = 9.75V$   $V_2 = 10.5V$