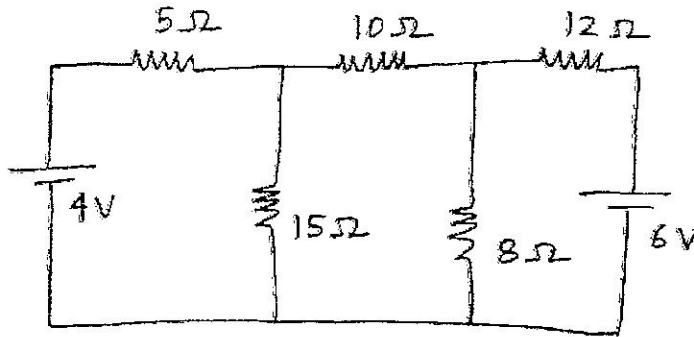


TUTORIAL NO.3

SUBJECT: B.E.E


TOPIC: SUPERPOSITION THEOREM

- Find the value of the current flowing through the  $8\Omega$  resistance using Superposition Theorem. (May 19)(8 m)




Ans.  $I_{8\Omega} = 0.319A(\downarrow)$ .

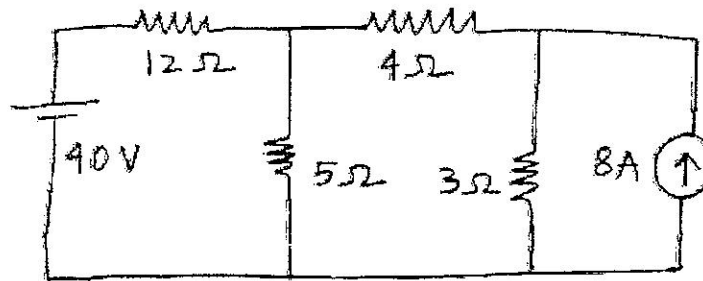- Find the value of the current flowing through the  $4\Omega$  resistance using Superposition Theorem. (May 19)(7 m)




Ans.  $I_{4\Omega} = 1.162A(\leftarrow)$ .

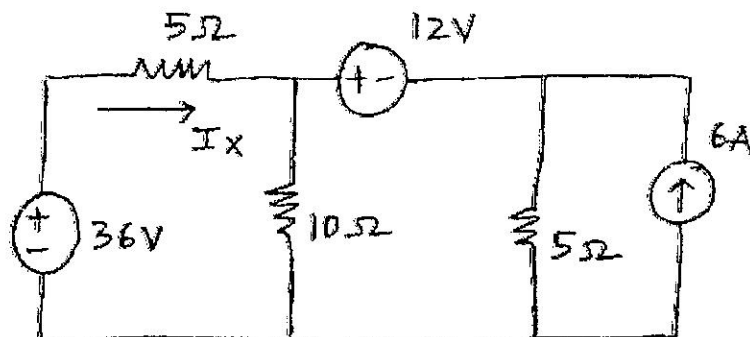- Find the value of the current  $I_X$  using Superposition Theorem. (Dec 18)(8 m)




Ans.  $I_X = 0.961A(\rightarrow)$ .

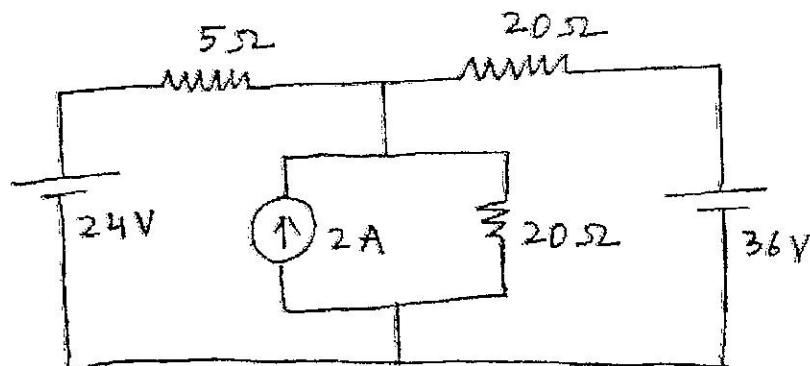4. Find the value of the current flowing through the  $5\Omega$  resistance using Superposition Theorem. (Dec 18)(7 m)




Ans.  $I_{5\Omega} = 0.934A(\leftarrow)$ .

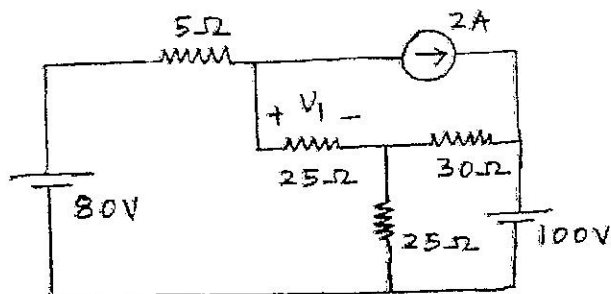5. Find  $V_1$  using Superposition Theorem. (May 18)(8 m)




Ans.  $V_1 = 14.062V$ .

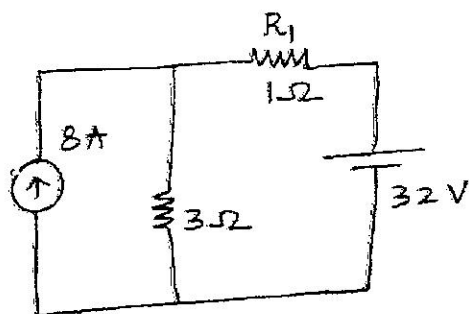6. Find the value of the current flowing through the  $R_1$  resistance using Superposition Theorem. (May 17)(8 m)




Ans.  $I_{1\Omega} = 2A(\leftarrow)$ .

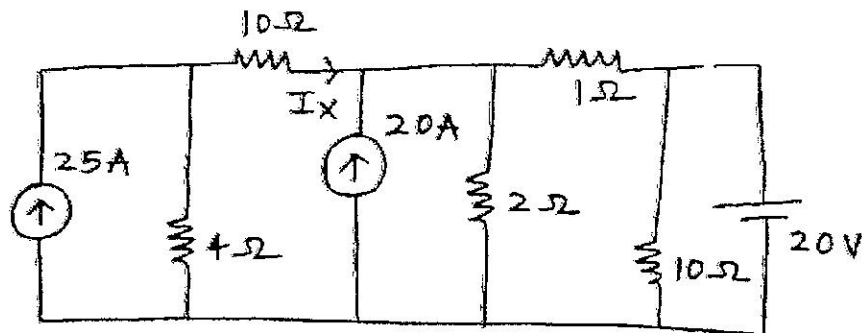7. State Superposition Theorem. Find  $I_X$  using superposition theorem without using source transformation. (Dec 17)(12 m)




Ans.  $I_X = 5A(\rightarrow)$ .

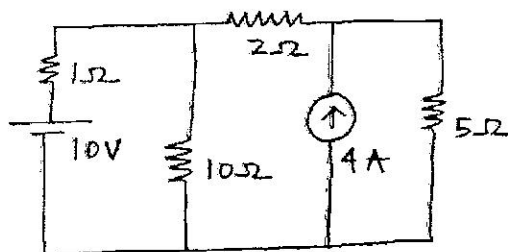8. Find the value of the current flowing through the  $10\Omega$  resistance using Superposition Theorem. (Dec 17)(7 m)




Ans.  $I_{10\Omega} = 1.034A(\downarrow)$ .

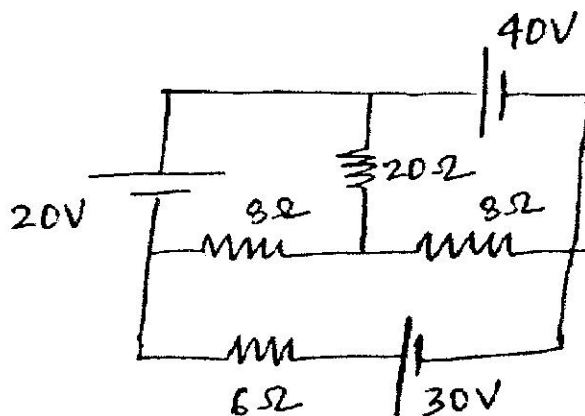9. Find the value of the current flowing through the  $20\Omega$  resistance using Superposition Theorem. (May 17)(8 m)




Ans.  $I_{20\Omega} = 1.25A(\downarrow)$ .

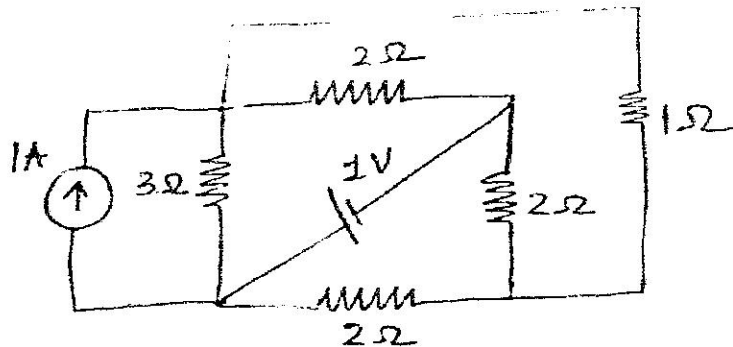10. Obtain current in  $1\Omega$  by using superposition theorem. (Dec 16)(10 m)




Ans.  $I_{1\Omega} = 0.34375A(\downarrow)$ .

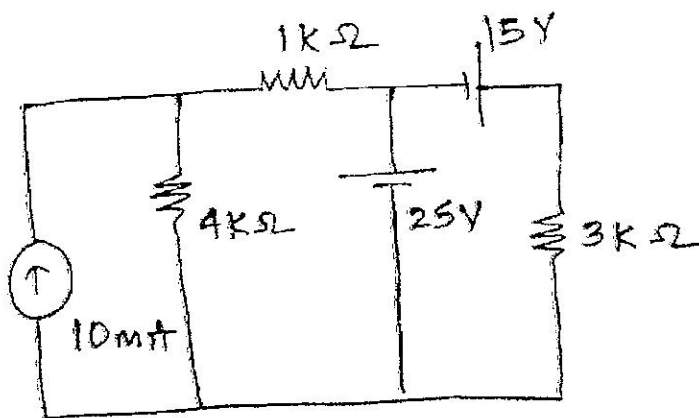11. Using Superposition theorem, voltage across  $4k\Omega$ . (May 16)(7 m)




Ans.  $V_{4k\Omega} = 28V$ .

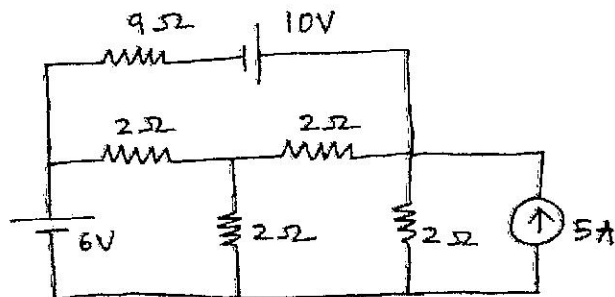12. Find the value of the current flowing through the  $9\Omega$  resistance using Superposition Theorem. (Dec 16)(7 m)




Ans.  $I_{9\Omega} = 0.8627A(\rightarrow)$ .

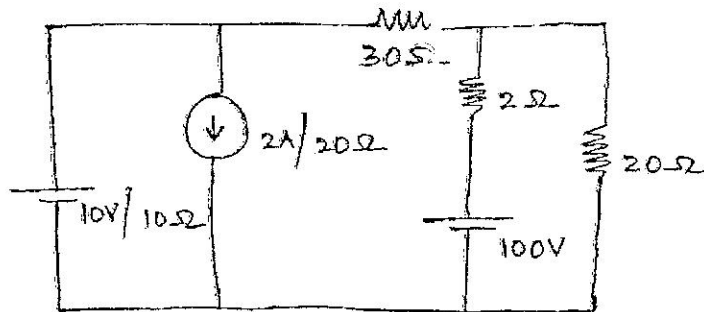13. Find the value of the current flowing through the  $30\Omega$  resistance using Superposition Theorem. (Dec 15)(7 m)




Ans.  $I_{30\Omega} = 2.5354A(\leftarrow)$ .

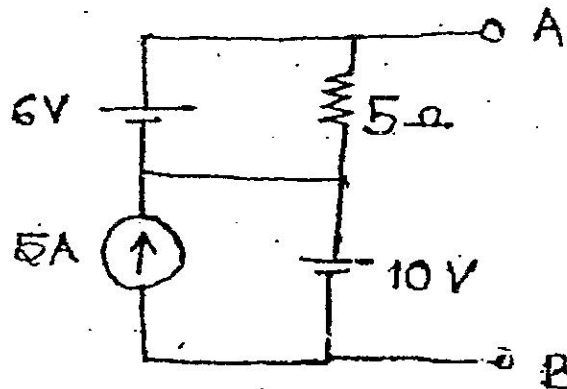14. For the above diagram, find voltage  $V_{AB}$  using superposition theorem. (Dec 14)(3 m)




Ans.  $V_{AB} = 16V$ .

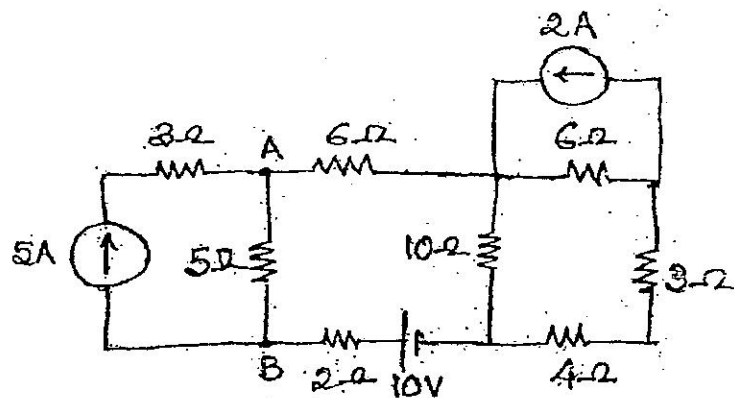15. Find the value of the current flowing through the  $5\Omega$  resistance using Superposition Theorem. (Dec 14)(7 m)




Ans.  $I_{5\Omega} = 3.4A(\downarrow)$ .

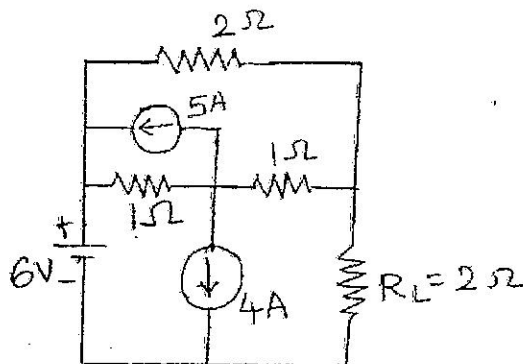16. Find the current through  $R_L = 2\Omega$  resistor by superposition theorem. (May 13) (7 m)




Ans.  $I_{2\Omega} = 0.5A(\downarrow)$ .

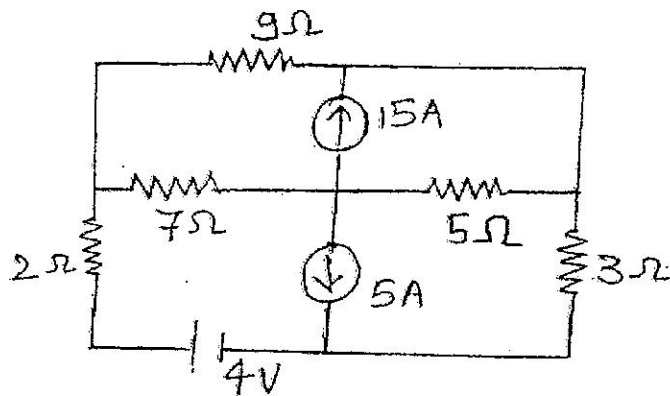17. Find the current through  $3\Omega$  resistor by superposition theorem. (Dec 12) (7 m)



Ans.  $I_{3\Omega} = 1.098A$ .

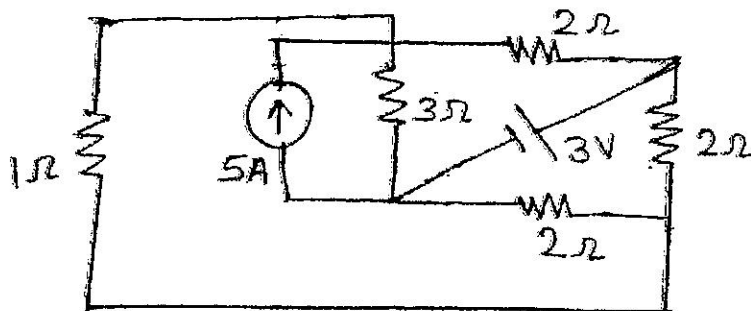18. Find the current through  $1\Omega$  resistor by superposition theorem. (Dec 12) (7 m)



Ans.  $I_{1\Omega} = 1.9688A(\downarrow)$ .