

FE DEPARTMENT

BEE INTERNAL ASSESMENT TEST II SOLUTIONS

B.E.E , IAT-II FE (All branches)


SOLUTION.

Q1. a.) given, $V(t) = 10 \sin(1000t) \text{ V}$

$V_{\text{max}} = 400 \text{ V}$ (capacitor peak voltage)

Quality factor $Q = \frac{V_C}{V_m} = \frac{V_{\text{max}}}{V_m} = \frac{400}{10} = 40$ (IM)

$\therefore Q = 40$ (IM)

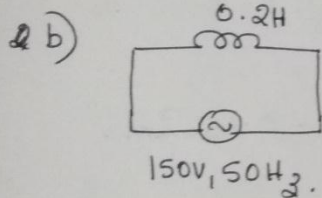

general equation for
voltage $V = V_m \sin \omega t$
current $I = I_m \sin \omega t$.

Given, $V_{\text{rms}} = 150 \text{ V}$; $V_m = \sqrt{2} \times 150 = 212.13 \text{ V}$


Inductance $L = 0.2 \text{ H}$

$X_L = 2\pi f L = 2 \times \pi \times 50 \times 0.2 = 62.83 \Omega$

$I_m = \frac{V_m}{X_L} = \frac{212.13}{62.83} = 3.37 \text{ A}$ (IM)

\therefore voltage $V = 212.13 \sin(314.15t)$ (IM)

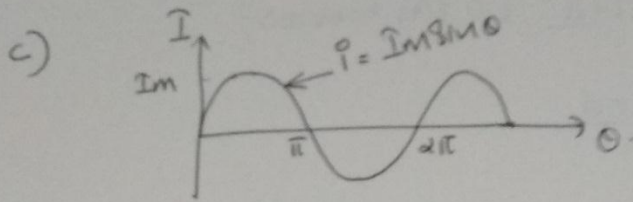current $I = 3.37 \sin(314.15t - \pi/2)$
(purely inductive).



$$i = I_m \sin \theta \quad 0 < \theta < 2\pi$$

Symmetrical waveform, average value is calculated over half cycle.


$$\therefore I_{avg} = \frac{1}{\pi} \int_0^{\pi} i(\theta) d\theta \quad [IM]$$

$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta d\theta = \frac{I_m}{\pi} [-\cos \theta]_0^{\pi}$$

$$I_{avg} = \frac{I_m}{\pi} [1+1] = \frac{2I_m}{\pi} = 0.636 I_m.$$

$$\boxed{I_{avg} = 0.636 I_m} \quad [IM]$$

d)

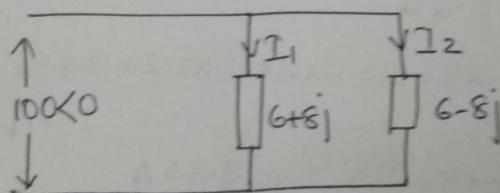


$$Z_1 = 6 + j8 = 10 \angle 53.13^\circ \Omega$$

$$Z_2 = 6 - j8 = 10 \angle -53.13^\circ \Omega$$

$$I_1 = \frac{V}{Z_1} = \frac{100 \angle 0^\circ}{10 \angle 53.13^\circ} = \underline{\underline{10 \angle -53.13^\circ \text{ A}}} \quad (6 - j7.99) \text{ A} \quad [IM]$$
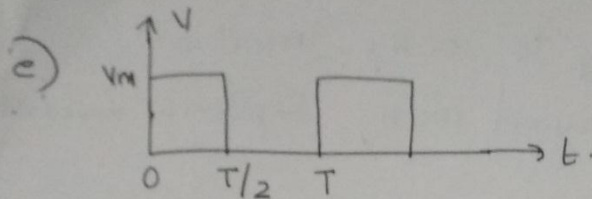
$$I_2 = \frac{V}{Z_2} = \frac{100 \angle 0^\circ}{10 \angle -53.13^\circ} = \underline{\underline{10 \angle 53.13^\circ \text{ A}}} \quad (6 + j7.99) \text{ A} \quad [IM]$$



$$V(t) = V_m \quad 0 < t < T/2 \quad [0.5M]$$

$$= 0 \quad T/2 < t < T.$$

$$V_{avg} = \frac{1}{T} \left[\int_0^{T/2} V_m dt + \int_{T/2}^T 0 dt \right] \quad [0.5M]$$


$$= \frac{1}{T} \times \int_0^{T/2} V_m dt.$$

$$= \frac{V_m}{T} \left[t \right]_0^{T/2}$$

$$V_{avg} = \frac{V_m}{T} \times \frac{T}{2} = \frac{V_m}{2} = 0.5 V_m \quad [1M]$$

$$\underline{\underline{V_{avg} = 0.5 V_m}}$$

f). Pure inductive circuit

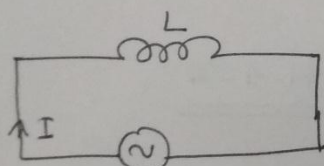

$$V = V_m \sin \omega t$$


phase difference $\phi = 90^\circ$

$$P.f = 0$$


$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - 90^\circ)$$


waveform

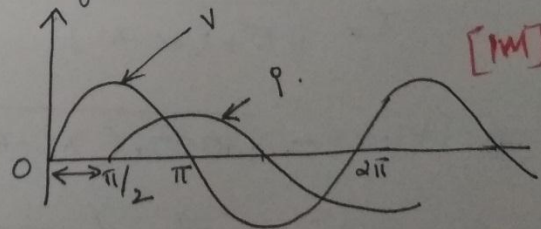

Phasor diagram

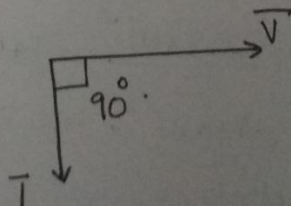

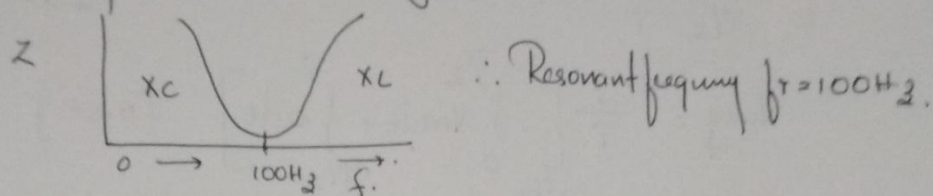2-a) given from 1 Hz to 100 Hz circuit is capacitive and beyond 100 Hz , impedance increases.



At resonance

$$f_r = 100\text{ Hz}$$

$$P = 100\text{ W}$$

$$I = 1\text{ A}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$P = VI \cos \phi$$


$$V = 100\text{ V}$$

$$R = \frac{V}{I} = \frac{100}{1} = 100\ \Omega$$

$$100 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow LC = 2.53 \times 10^{-6} \text{ --- (1)}$$

[2M]

Case II At 70 Hz , $\cos \phi = 0.707$

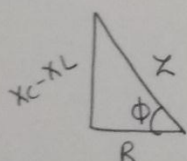

$$\cos \phi = \frac{R}{Z}$$

$$Z = \frac{R}{\cos \phi} = \frac{100}{0.707} = \underline{\underline{141.4\ \Omega}}$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\Rightarrow 141.44 = \sqrt{100^2 + (X_C - X_L)^2}$$

$$\Rightarrow (141.44)^2 = 100^2 + \left(\frac{1}{2\pi \times 70 \times C} - 2\pi \times 70 \times L \right)^2$$

$$\Rightarrow 100.02 = \frac{2.243 \times 10^{-3}}{C} - 140\pi L$$

$$\Rightarrow 100.02 C = 2.243 \times 10^{-3} - 140\pi LC \text{ --- (2)}$$

Substitute (1) in (2)

$$\Rightarrow 100.02 C = 2.243 \times 10^{-3} - 140\pi [2.53 \times 10^{-6}]$$

$$\Rightarrow C = \frac{1.1602 \times 10^{-3}}{100.02}$$

$$C = 11.59 \mu F$$

[2M]


$$\text{eq ①} \Rightarrow LC = 2.53 \times 10^{-6}$$

$$L = \frac{2.53 \times 10^{-6}}{11.59 \times 10^{-6}} = 0.218 H$$

[1M]

$$\begin{array}{l} L = 11.59 \mu F \\ C = 0.218 H \\ R = 100 \Omega \end{array}$$

2 b)

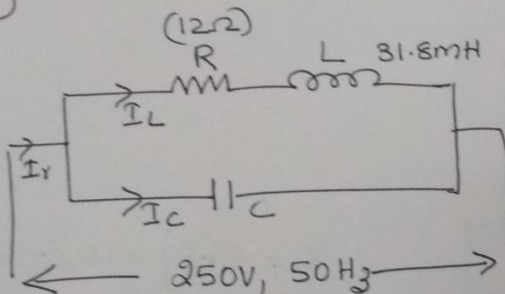

The given parallel circuit is in resonance at $50 Hz$.

$$\therefore f_r = 50 Hz.$$

[\therefore net reactive current is zero].

$$\text{Given; } R = 12 \Omega$$

$$L = 31.8 mH; X_L = 2\pi f L = 2\pi \times 50 \times 31.8 \times 10^{-3}$$

$$X_L = 9.99 \Omega$$

[1M]

$$V = 250 V$$

$$f_r = 50 Hz.$$

$$\text{At resonance; } I_C = I_L \sin \phi_L.$$

$$Z_L = \sqrt{R^2 + X_L^2} = \sqrt{12^2 + 9.99^2} = 15.61 \Omega$$

$$P.f_L = \cos \phi_L = \frac{R}{Z_L} = \frac{12}{15.61} = 0.7687$$

$$\text{current } I_L = \frac{V}{Z_L} = \frac{250}{15.61} = \underline{\underline{16.01A}} \quad [2M]$$

$$\therefore I_C = I_L \sin \phi_L$$

$$I_C = 16.01 \sin(39.75) = \underline{\underline{10.23A}}$$


$$X_C = \frac{V}{I_C} = \frac{250}{10.23} = \underline{\underline{24.43\Omega}} \quad [2M]$$

$$X_C = \frac{1}{2\pi f C}$$

$$\therefore C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 24.43} = \underline{\underline{130.29\mu F}}$$

$$C = 130.29\mu F$$

3a).

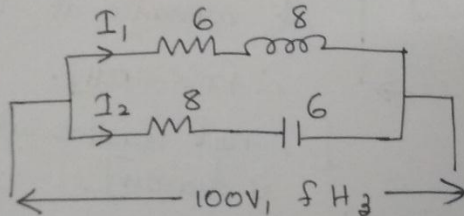

$$Z_1 = 6 + 8j = 10 \angle 53.13^\circ \Omega$$

$$Z_2 = 8 - 6j = 10 \angle -36.86^\circ \Omega$$

Branch ①

$$I_1 = \frac{V}{Z_1} = \frac{100 \angle 0}{10 \angle -53.13} = 6 - 8j = 10 \angle -53.13^\circ \text{ A} \quad [2.5M]$$

$$\text{P.f of branch 1 } \cos \phi_1 = \cos(53.13) = \underline{\underline{0.6 \text{ lagging}}}$$


$$\text{Power consumed } P_1 = I_1^2 R = 10^2 \times 6 = \underline{\underline{600W}}$$

Branch ②

$$I_2 = \frac{V}{Z_2} = \frac{100 \angle 0}{10 \angle -36.86} = 8 + 6j = 10 \angle 36.86^\circ \text{ A}$$

P.f of branch 2 $\cos \phi_2 = \cos(36.86) = 0.8$ leading.

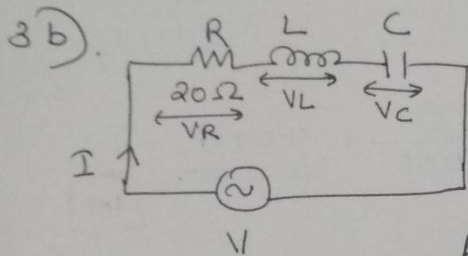Power consumed by branch 2 $P_2 = I_2^2 R$ [2.5M]
 $P_2 = 10^2 \times 8 = 800 \text{ W}$



given; current lags behind voltage by 45° ; inductive circuit.
 $\therefore X_L > X_C$; $\phi = 45^\circ$.

Also given; $V_{L\text{max}} = 2 V_{C\text{max}}$.

$$V_L = 300 \sin(1000t)$$

$$R = 20 \Omega$$

$$V_{L\text{max}} = 2 V_{C\text{max}} \quad (V_{\text{rms}} = \frac{1}{\sqrt{2}} V_{\text{max}})$$

$$\sqrt{2} V_{L\text{max}} = \sqrt{2} \times 2 V_{C\text{max}}$$

$$V_L = 2 V_C$$

$$I X_L = 2 I X_C$$

$$X_L = 2 X_C \quad \text{--- ①}$$

given $\phi = 45^\circ$; $\cos \phi = \cos 45$

$\cos(45) = \frac{R}{Z} \Rightarrow Z = \frac{R}{\cos 45} = \frac{20}{0.707} = 28.28 \Omega$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$28.28 = \sqrt{20^2 + (2X_C - X_C)^2} \quad \therefore X_L = 2X_C$$

$$(28.28)^2 = 20^2 + X_C^2$$

$$\underline{\underline{X_C = 19.99 \approx 20 \Omega}}$$

[2M]

$$X_L = 2X_C = 2 \times 20 = \underline{\underline{40 \Omega}}$$

given $\omega = 1000 \text{ rad/sec}$

$$X_L = 2\pi f L$$

$$\Rightarrow L = \frac{X_L}{2\pi f} = \frac{40}{1000} = \underline{\underline{0.04 \text{ H}}}$$

[1M]

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{1000 \times 20} = \underline{\underline{50 \mu\text{F}}}$$

$L = 0.04 \text{ H}$ $C = 50 \mu\text{F}$
