


IAT-1 SOLUTION SET.

my companion

(1)


Q1.

- (a) Find R_{AB} for the following n/w.

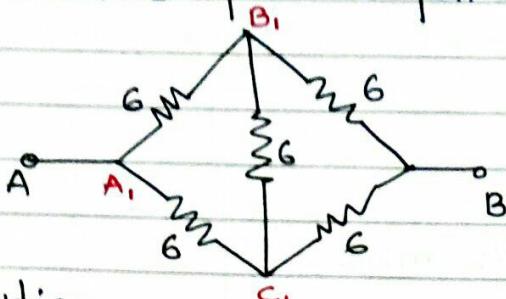


Solution

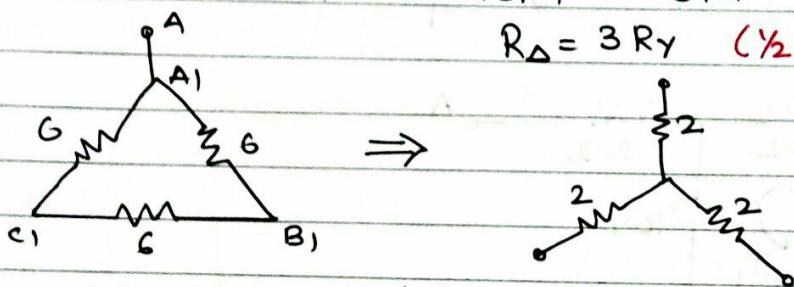convert the delta A_1, B_1, C_1 , to star n/w.




$$R_\Delta = 3 R_y \quad (\frac{1}{2} \text{ m}\Omega)$$

\therefore The ckt reduces to

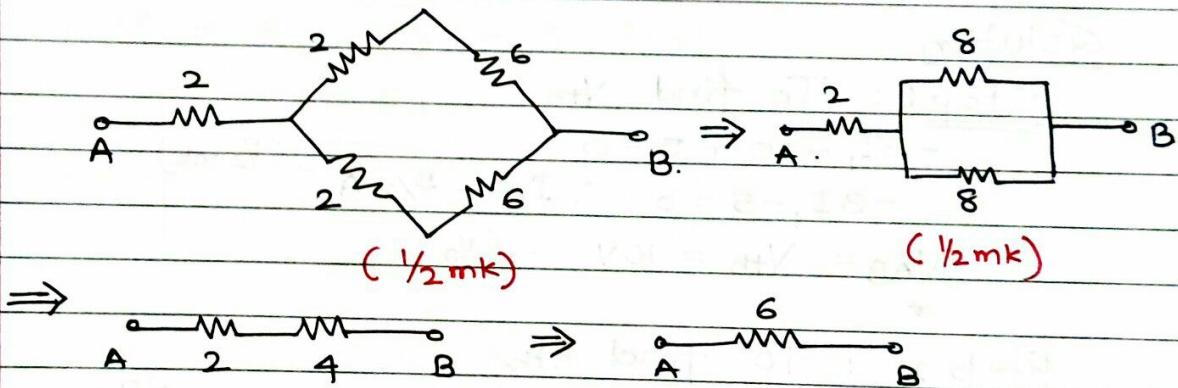

$$\therefore R_{AB} = 6 \Omega \quad (\frac{1}{2} \text{ m}\Omega)$$

- (b) Find Mesh currents in the ckt's

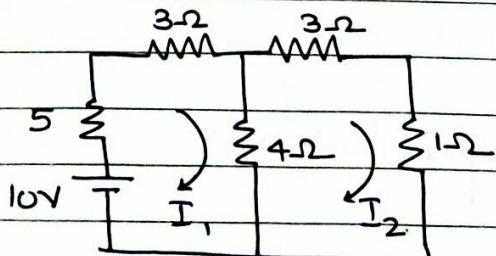

Mesh-2

$$-3I_2 - 1I_2 - 4(I_2 - I_1) = 0$$

$$\therefore -3I_2 - I_2 - 4I_2 + 4I_1 = 0$$

$$\therefore 4I_1 - 8I_2 = 0$$

$$\therefore I_1 - 2I_2 = 0 \quad \text{--- (1)}$$

Mesh 1

$$-3I_1 - 4(I_1 - I_2) + 10 - 5I_1 = 0$$

$$\Rightarrow -3I_1 - 4I_1 + 4I_2 - 5I_1 + 10 = 0$$

$$\Rightarrow -12I_1 + 4I_2 + 10 = 0$$

$$\Rightarrow 12I_1 - 4I_2 = 10 \quad \text{--- (1)}$$

$$(\frac{1}{2} \text{ m}\Omega)$$

$$\times \text{Eq. (1)} \text{ by } I_2 \quad (\frac{1}{2} \text{ m}\Omega)$$

$$12I_1 - 24I_2 = 0$$

$$12I_1 - 4I_2 = 10$$

$$-20I_2 = -10 \quad (\text{P.T.})$$


$$\therefore I_2 = \frac{10}{20} = 0.5 \text{ A. } (\frac{1}{2} \text{ mK})$$

put I_2 in Eq ⑪

$$\therefore I_1 = 2I_2 \\ = 2(0.5)$$

$$\underline{I_1 = 1 \text{ A. } (\frac{1}{2} \text{ mK})}$$

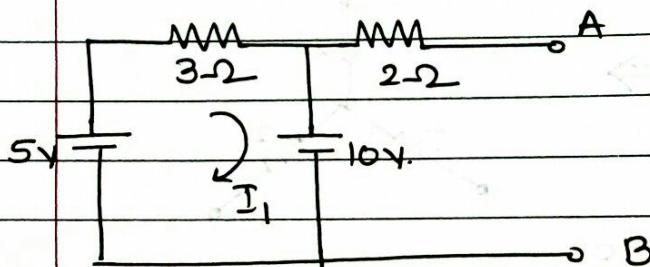(c) Draw thevenin's equivalent ckt across A and B.



Solution


Step 1 : To find V_{th}

$$-3I_1 - 10 + 5 = 0$$

$$\therefore -3I_1 - 5 = 0 \quad \therefore I_1 = -5/3 \text{ A. } (-\frac{1}{2} \text{ mK})$$


$$V_{AB} = V_{th} = 10V - (\frac{1}{2})$$

Step 2 : To find R_{th}

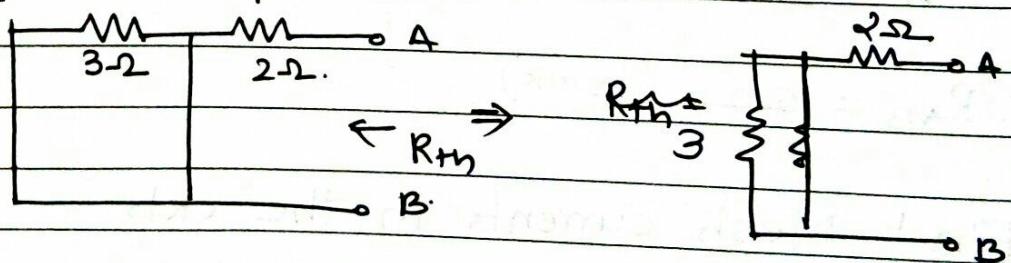


$$\therefore R_{th} = 2\Omega. (\frac{1}{2} \text{ mK})$$

Step 3 Thevenin's equivalent ckt.

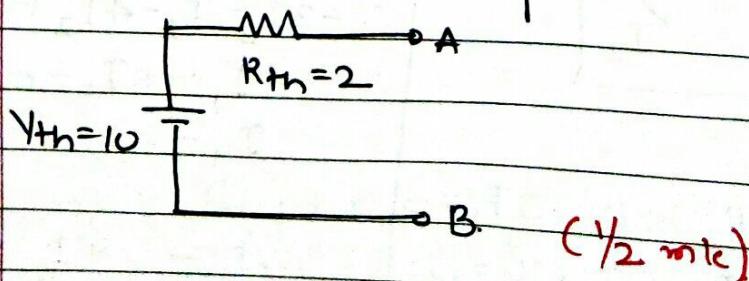

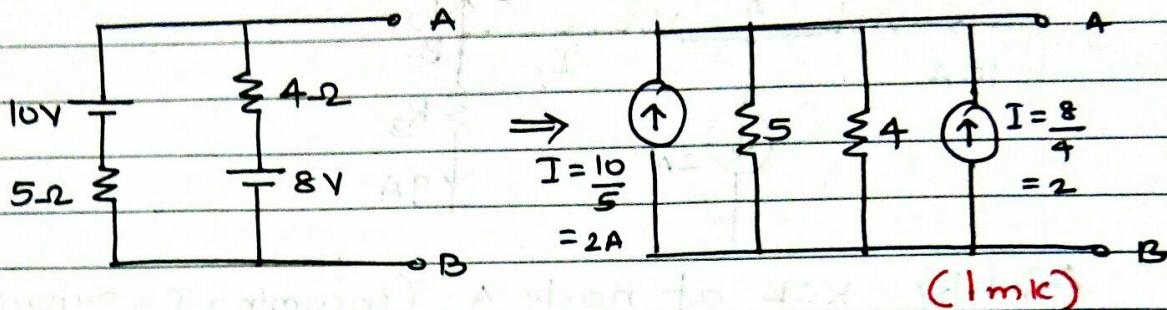(d) Convert the given circuit to single v.tg. source in series with a single resistor




Currents in ||a|| can be added.

$$R_{eq} = (5/14)$$

$$R_{eq} = \frac{5 \times 4}{5+4} = \frac{20}{9} = 2.22\Omega$$

$(1/2\text{ m}\Omega)$
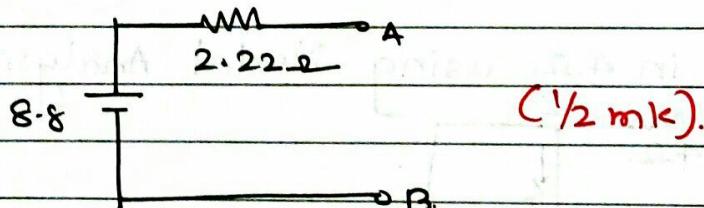
$$V = IR = 4 \times 2.22 = 8.88\text{ Volts}$$



(e) An alternating current is given by $i(t) = 141.4 \sin(314t)$. Find the maximum value of current and frequency.

Solution

$$i(t) = 141.4 \sin(314t) \quad \text{--- (1) ... given}$$

$$i(t) = I_m \sin(\omega t) \quad \text{--- (2) ... standard form}$$

Compare (1) & (2)


(a) $I_m = 141.4 \text{ Amps.} \quad (1\text{ m}\Omega)$

(b) $\omega = 314$

$$2\pi f = 314$$

$$\therefore f = \frac{314}{2 \times \pi} = \frac{314}{2 \times 3.14} = 50\text{ Hz} \quad (1/2\text{ m}\Omega)$$

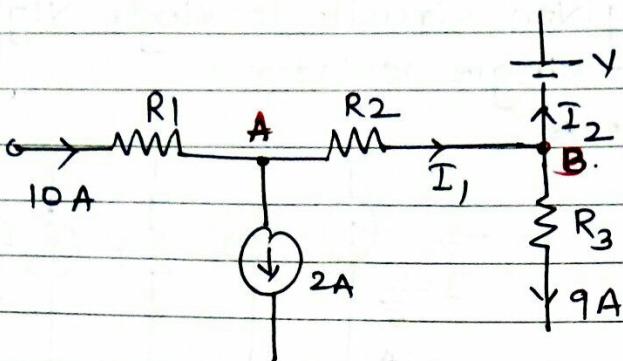(f.) Find the unknown currents using KCL.



Apply KCL at node A. (incoming $I =$ outgoing I)

$$10 = 2 + I_1$$

$$\therefore I_1 = 8 \text{ A. } \text{(Ime)}$$


Apply KCL at node B.

$$I_1 = I_2 + 9$$

$$8 = I_2 + 9 \quad \text{(Ime).}$$

$$\therefore I_2 = 8 - 9 = -1 \text{ A. } \text{(Direction is opposite to the marked)}$$

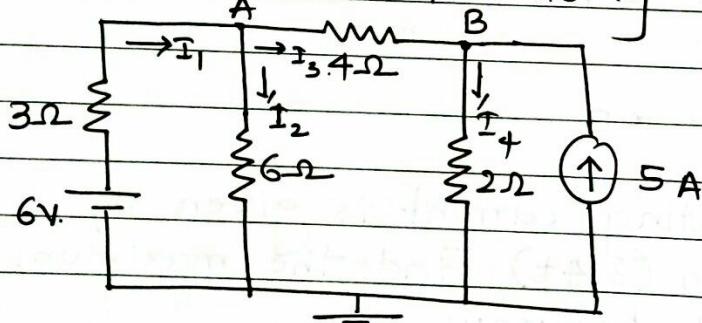2. a) Find current in 4Ω using Nodal Analysis.



Apply KCL at node A.

$$\frac{6 - V_A}{3} = \frac{V_A}{6} + \frac{V_A - V_B}{4}$$

$$\therefore \frac{2 - V_A}{12} + \frac{V_B}{4} = 0$$

$$\Rightarrow 2 - \frac{V_A}{3} - \frac{V_A}{6} - \frac{V_A}{4} + \frac{V_B}{4} = 0$$

$$\therefore 2 = \frac{3}{4}V_A - \frac{1}{4}V_B. \quad \text{---(1)}$$

$$\Rightarrow 2 - V_A \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{4} \right) + \frac{V_B}{4} = 0$$

$$\Rightarrow 2 - V_A \left(\frac{4+2+3}{12} \right) + \frac{V_B}{4} = 0$$

$$\Rightarrow 2 - \frac{V_A}{9} + \frac{V_B}{4} = 0$$

$$\therefore \frac{1}{9}V_A - \frac{1}{4}V_B = 2$$

$$-\frac{1}{4} + \frac{1}{4} = 0$$

my companion

(2)

Apply KCL at node B.

$$\frac{V_A - V_B}{4} + 5 = \frac{V_B}{2}$$

~~$$\Rightarrow \frac{V_A - V_B}{4} - \frac{V_B}{2} = -5$$~~

$$\Rightarrow \frac{V_A}{4} - V_B \left(\frac{1}{4} + \frac{1}{2} \right) = -5$$

$$\Rightarrow \frac{V_A}{4} - V_B \left(\frac{1+2}{4} \right) = -5$$

$$\Rightarrow \frac{V_A}{4} - \frac{3}{4} V_B = -5 \quad \text{(11)}$$

$$V_A = 1/2 \quad \frac{9}{4} - \frac{1}{4} = \frac{8}{2}$$

$$V_B =$$

put in Eq ①

$$\frac{3}{4} V_A - \frac{1}{4} V_B = 2$$

$$\frac{3}{4} V_A - \frac{1}{4} \times \frac{17}{2} = 2$$

$$\frac{3}{4} V_A = 2 + \frac{17}{8}$$

$$= \frac{16+17}{8}$$

$$\frac{3}{4} V_A = \frac{33}{8}$$

$$\therefore V_A = \frac{33}{8} \times \frac{4}{3}$$

$$V_A = \frac{35}{6} \quad 10/18$$

$$\frac{3}{4} V_A - \frac{1}{4} V_B = 2 \quad \text{--- ①}$$

$$\frac{1}{4} V_A - \frac{3}{4} V_B = -5 \quad \text{--- 11} \times 3$$

$$\frac{3}{4} V_A - \frac{1}{4} V_B = 2$$

$$\frac{3}{4} V_A - \frac{9}{4} V_B = -15$$

$$2 V_B = +17$$

$$V_B = \underline{\underline{17/2}}$$

$$I_{4-2} = \frac{V_A - V_B}{4}$$

$$= \frac{\frac{11}{2} - \frac{17}{2}}{4}$$

~~$$-0.66 A$$~~

$$I_{4\bar{2}} = -0.75 A$$

$$I_{4\bar{2}} = 0.75 A (\leftarrow)$$

$$V_A = \frac{33 \times 4}{8 \times 3} = \frac{11}{2} V$$


V_A cal. → 2 mV

V_B cal → 2 mV


$$I_{4\bar{2}} = 1 mA$$

(P.T.O.)

(b) Find current in 15Ω using S.T.

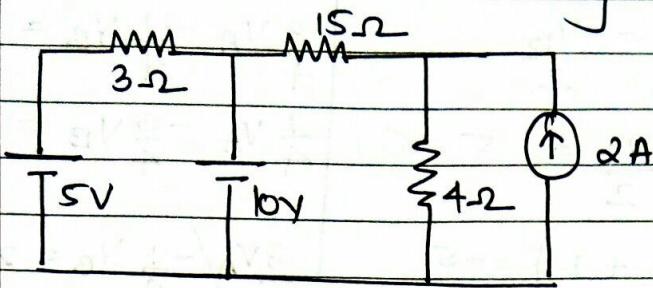


Consider 5V supply (1m μ)

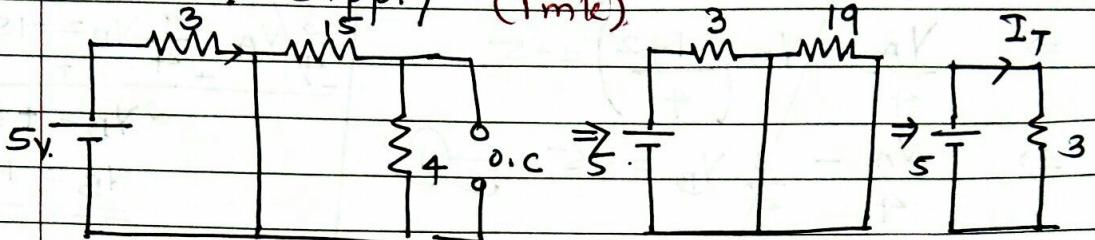

$$I_T = \frac{R_{eq}}{R_{eq}} \cdot \frac{V}{R_{eq}} = \frac{5}{3} \text{ Amp} = 1.66 \text{ A}$$

$\therefore I_{15\Omega} = 0 \text{ Amp} \rightarrow (\text{because of s.c.})$

consider 10V supply (1m μ)

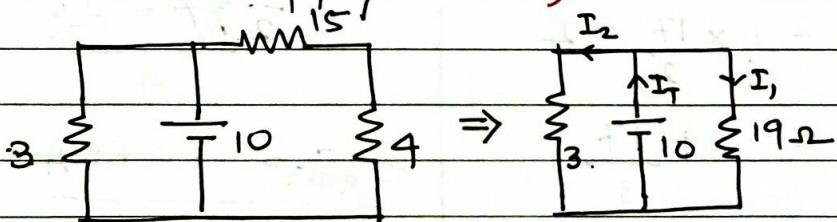


$$R_{eq} = \frac{19 \times 3}{19 + 3} = 2.59 \quad \therefore I_T = \frac{10}{2.59} = 3.85 \text{ A}$$


$$\therefore I_1 = 3.85 \times \frac{3}{19+3} = 0.526$$

$\therefore (I_{15}) = 0.526 \rightarrow \text{Amp}$

Consider 2A current source. (1m μ)

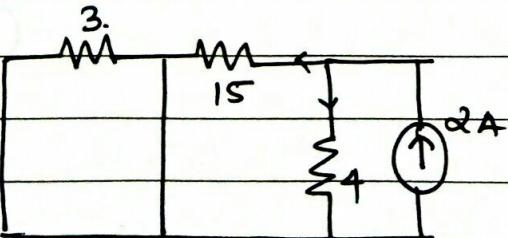
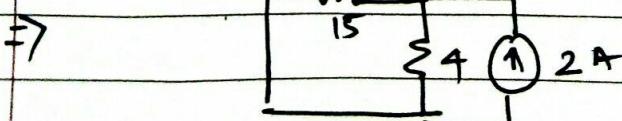
$$I_{15} = 2 \times \frac{4}{19} = \frac{8}{19} = 0.421 \leftarrow$$




$$\therefore (I_{15}) = (I_{15})_{5} + (I_{15})_{10v} + (I_{15})_{24}$$


$$= 0 + 0.526(\rightarrow) + 0.421(\leftarrow)$$

$$(I_{15})_n = 0.105(\rightarrow) \text{Amp (1mK)}$$

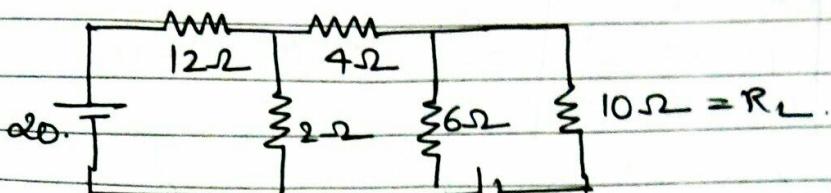Q3(a) Find current in 10Ω using Norton's Analysis.



Step 1 : Find s.c current I_N . (2mK).

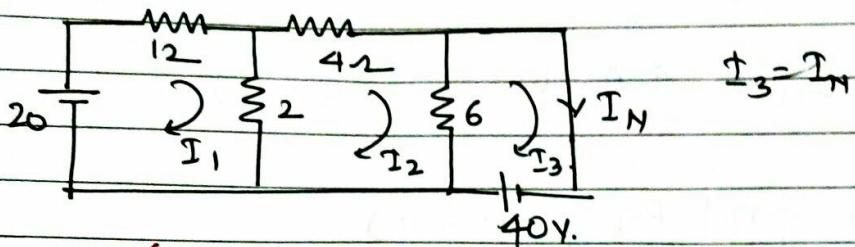

Mesh 1 (1mK)

$$-12I_1 - 2(I_1 - I_2) + 20 = 0$$

$$\Rightarrow -12I_1 - 2I_1 + 2I_2 + 20 = 0$$

$$\Rightarrow -14I_1 + 2I_2 = -20$$

$$\Rightarrow 7I_1 - I_2 = 10 \quad \textcircled{1}$$

Mesh 2 (1mK)

$$-4I_2 - 6(I_2 - I_3) - 2(I_2 - I_1) = 0$$

$$\Rightarrow -4I_2 - 6I_2 + 6I_3 - 2I_2 + 2I_1 = 0$$

$$\Rightarrow 2I_1 - 12I_2 + 6I_3 = 0$$

$$\Rightarrow I_1 - 6I_2 + 3I_3 = 0 \quad \textcircled{II}$$

Mesh 3 (1mK)

$$40 - 6(I_3 - I_2) = 0$$

$$\Rightarrow -6I_3 + 6I_2 = -40$$

$$\Rightarrow 6I_2 - 6I_3 = -40$$

$$\Rightarrow 3I_2 - 3I_3 = -20 \quad \textcircled{III}$$

In matrix form it can be written as -

$$\begin{bmatrix} 7 & -1 & 0 \\ 1 & -6 & 3 \\ 0 & 3 & -3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -20 \end{bmatrix}$$

my companion

$$\Delta = 7(-6 \times -3) - 9 + 1(-3 - 0) + 0.$$

$$\Delta = 7(9) - 3 = 60$$

$$\Delta_3 = \begin{vmatrix} 7 & -1 & 10 \\ 1 & -6 & 0 \\ 0 & 3 & 20 \end{vmatrix} = \Delta_{3 \text{ mle}}$$


$$= 7(-6 \times 20 - 0) - 1(20 - 0) + 10(3 - 0)$$

$$= 7(-120) - 20 + 30.$$

$$= -830.$$


$$I_3 = I_N \approx \underline{14 \text{ Amp}} \quad - 0.5 \text{ mle}.$$

Step 2 To find R_N . (2mle)

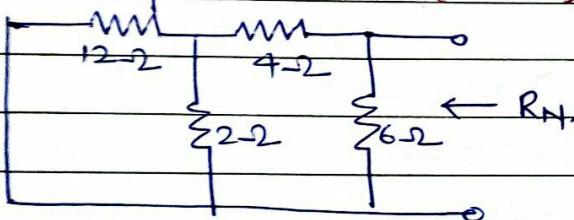


$$\therefore R_N = \left\{ [12/12] + 4 \right\} / 16 = 2.92 \Omega.$$

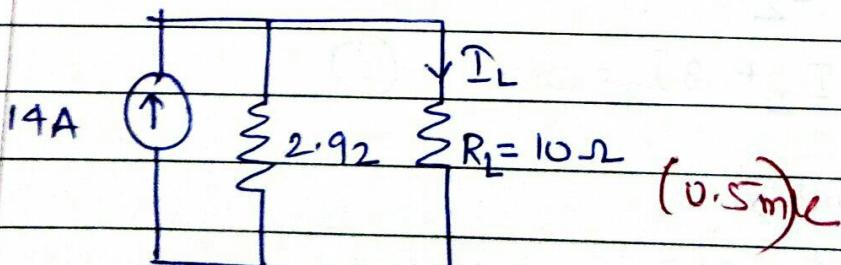Step 3 : To draw the Norton Equivalent ckt
find $I_{10 \Omega}$. (1mle).





$$\therefore I_L = 14 \times \frac{2.92}{10 + 2.92} = \underline{\underline{3.18 \text{ A}}} \quad (0.5 \text{ mle}).$$

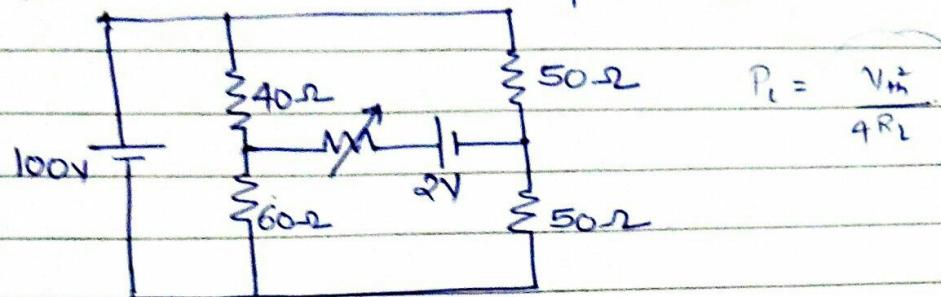Q3(b) Find maximum power delivered load R_L . *my companion*



$$P_L = \frac{V_m^2}{4R_L}$$

Step 1 : To find R_{th} (2mk)

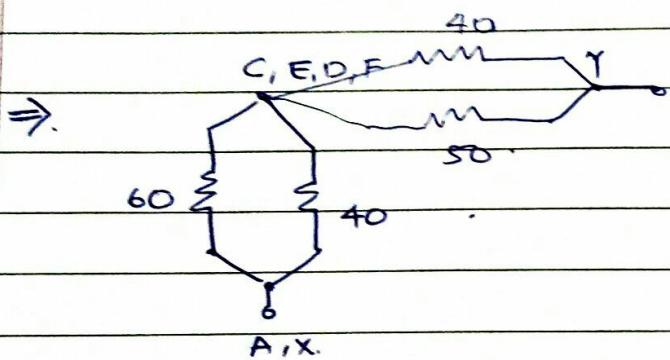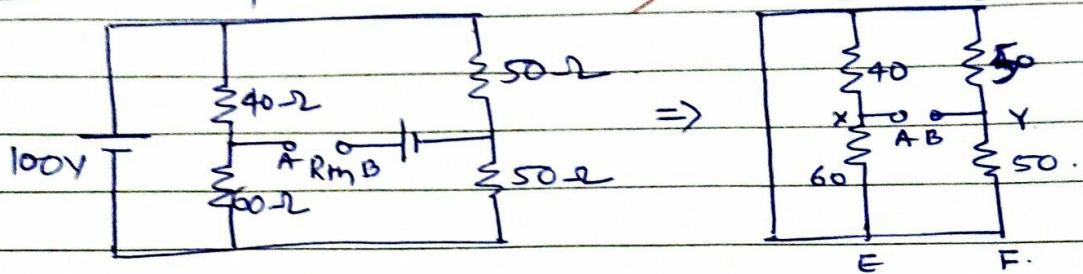

$$60//40 = \frac{40 \times 60}{40 + 60} = \frac{2400}{100} = 24\Omega$$

$$50//50 = \frac{50 \times 50}{50 + 50} = \frac{2500}{100} = 25\Omega$$

$$\therefore R_{th} = \frac{40+24+25}{3} = 49\Omega$$

$$V_{th} = 8V. \quad (2mk)$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{8 \times 8}{4 \times 49} = \frac{64}{196} = 0.326 \text{ Watts}$$

$$\therefore P_{max} = 0.326 \text{ Watts} \quad (1mk)$$

—X— X—