

Q.1. Attempt any five. ( $2 \times 5 = 10$ )

(a)  $C = 314 \mu F$ ,  $V = 230 V$ .  
 $f = 50 \text{ Hz}$ ,  $1-\phi$  A.C. supply.  
 $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 314 \times 10^{-6}} = 10.137 \Omega$  (IM)  
 $I = \frac{230}{10.137} = \frac{V}{X_C} = 22.688 \text{ A}$  (IM)

(b)  $v(t) = 282.85 \sin(100\pi t) \text{ V}$ .

$\omega = 100\pi \text{ radian/sec}$


$X_L = 2\pi f L = \omega L = 100\pi \times 31.83 \times 10^{-3}$

$= 9.999 \Omega$

$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{20^2 + 9.99^2} \Omega$

$Z = R + jX_L = 20 + j9.99 \Omega$

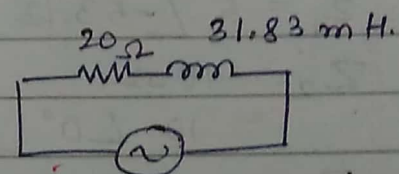$Z = 22.35 \angle 26.54^\circ \Omega$  (IM)




$v(t) = 282.85 \sin(100\pi t)$

$V_m = 282.85 \text{ V}$

$V_{rms} = 200.0 \text{ V}$

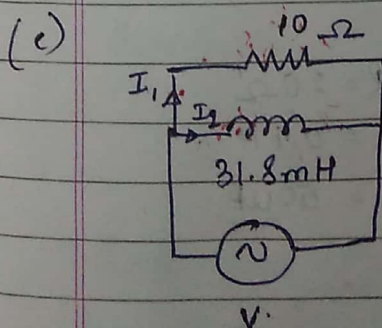$I = \frac{V_{rms}}{Z} = \frac{200}{22.35 \angle 26.54} = 8.948 \angle -26.54 \text{ A}$  (IM)



$V = 200 \text{ V}$

$f = 50 \text{ Hz}$

$X_L = 2\pi f L = 9.99 \Omega$

$I = ?$

$P \cdot f = ?$

$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L} = \frac{1}{10} + \frac{1}{j9.99}$

$\frac{V}{Z} = I_1 = \frac{200 \angle 0}{10} = 20 \angle 0 \text{ A}$

$I_2 = \frac{200 \angle 0}{9.99 \angle 90} = 20 \angle -90^\circ \text{ A}$

$I = I_1 + I_2 = 20 - j20 = 28.28 \angle -45.0^\circ \text{ A} = 28.28 \angle -45^\circ$

$$I = 28.28 \angle -45.00^\circ \text{ A} \quad \text{--- } 28.28 \angle -45^\circ \text{ A} \quad \text{--- (1M)}$$

power factor =  $\cos(-45.00^\circ)$   
 = 0.707 lagging. --- (1M)

(d) Find current  $I_1$  and  $I_2$ .

$$Z_1 = 3 - j4 \Omega$$

$$Z_1 = 5 \angle -53.13^\circ \Omega$$

$$Z_2 = 10 \Omega$$

$$= 10 \angle 0^\circ \Omega$$

$$Z_1 + Z_2 = 3 - j4 + 10 = 13 - j4 = 13.6 \angle -17.10^\circ \Omega$$

$$I_1 = \frac{I \times Z_2}{Z_1 + Z_2}$$


$$= \frac{(25 \angle 90^\circ) \times (10 \angle 0^\circ)}{(13.6 \angle -17.10^\circ)}$$

$$I_1 = 18.38 \angle 107.1^\circ \text{ A} \quad \text{--- (1M)}$$

$$I_2 = \frac{I \times Z_1}{Z_1 + Z_2}$$

$$= \frac{25 \angle 90^\circ \times (5 \angle -53.13^\circ)}{(13.6 \angle -17.10^\circ)}$$
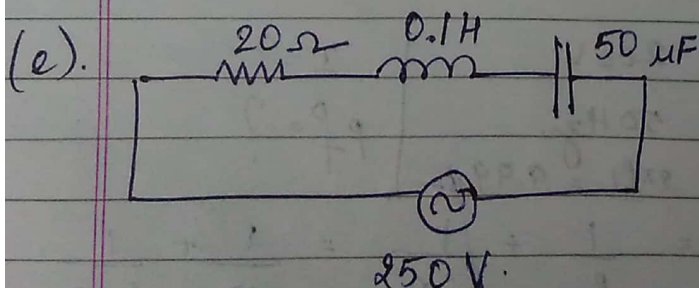
$$I_2 = 9.19 \angle 53.13^\circ \text{ A} \quad \text{--- (1M)}$$



$$R = 20 \Omega$$

$$L = 0.1 \text{ H}$$

$$C = 50 \mu\text{F}$$

The current will be maximum at resonant frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 50 \times 10^{-6}}} = 71.17 \text{ Hz} \quad \text{--- (2M)}$$



(4) Series ResonanceParallel Resonance.

(i) Impedance at Resonance  
 $Z = R$  and is minimum.

Impedance at resonance  
 $Z = \frac{L}{CR}$  and is maximum. (1/2M)

(ii) Current at resonance  
 $I = \frac{V}{R}$ , is maximum.

Current at resonance  
 $I = \frac{VCR}{L}$ , is minimum. (1/2M)

(iii)  $Q = \frac{\text{Voltage across Inductor or Capacitor}}{\text{Voltage at Resonance}}$

$Q = \frac{\text{Current through Inductor or Capacitor}}{\text{Current at Resonance}}$


$$= \frac{2\pi f L}{R}$$

It magnifies voltage across L and C

$$= \frac{2\pi f L}{R}$$

It magnifies current through L and C.

Q.2(a)

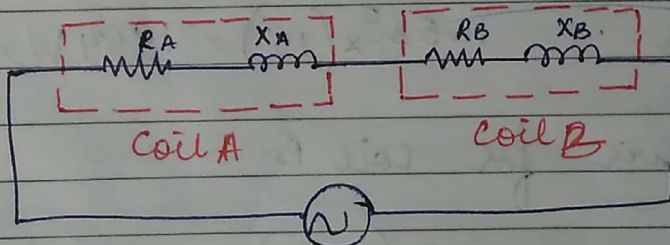

200V, 50Hz supply.

$$R_A = 5 \Omega$$

$$X_A = 8 \Omega$$

$$R_B = ?$$

$$X_B = ?$$

$$P = 2 \text{ kW}$$

$$Q = 1.15 \text{ KVAR.}$$

$$\tan \phi = \frac{Q}{P} = \frac{1.15}{2} = 0.575$$

$$\phi = \tan^{-1}(0.575) = 29.89^\circ$$

$$\text{Apparant Power } S = \sqrt{P^2 + Q^2} = \sqrt{2^2 + 1.15^2} = 2307.05 \text{ VA}$$

$$\therefore I = \frac{S}{V} = \frac{2307.05}{200} = 11.53 \angle -29.89^\circ \text{ A.}$$

Now

$$\text{total Impedance } Z = \frac{V}{I} = \frac{200 \angle 0}{11.53 \angle -29.89}$$

$$\therefore Z = 17.34 \angle 29.89^\circ \Omega$$



$$R_{TOTAL} = R_A + R_B = Z \cos \phi = 17.34 \cos(-29.89^\circ)$$

$$= 15.03 \Omega$$

$$\therefore R_B = 15.03 - 5 = \boxed{10.03 \Omega}$$

$$X_{TOTAL} = Z \sin \phi = 17.34 \sin(-29.89^\circ) = 8.641 \Omega$$

$$= X_A + X_B$$

(Inductive)  
coil.

$$\therefore X_B = 8.641 - 8 = \boxed{0.641 \Omega}$$

$$V_A = V_{RA} + j V_{XA}$$

$$V_{RA} = 11.53 \times 5 = 57.65 V$$

$$V_{XA} = 11.53 \times 8 = 92.24 \Omega$$

Active power of coil A

$$P_A = 57.65 \times 11.53 = 664 W$$

Reactive power of coil B

$$Q_A = 92.24 \times 11.53 = 1063.5 \text{ VAR}$$

$$\frac{R_A}{X_A} = \frac{5}{8} \Rightarrow \tan \phi = 5/8$$

$$\text{pf} = \cos \phi = \cos 57.99^\circ$$

$$\cos \phi_A = \text{power factor} = \cos 57.99^\circ$$

$$= 0.527 = 0.52$$

lag.

$$V_B = V_{RB} + j V_{XB}$$

$$V_{RB} = 11.53 \times 10.03$$

$$= 115.6 V$$

$$V_{XB} = 11.53 \times 0.641$$

$$= 7.39 V$$

$$P_B = 11.53 \times 115.6 = 1333 W$$

$$= 1333.78 W \text{ (Active Power)}$$

$$Q_B = 11.53 \times 7.39$$

$$= 85.206 \text{ VAR}$$

Reactive power of coil B


$$\frac{R_B}{X_B} = \frac{10.03}{0.641} = 15.647$$

$$\phi_B = 86.34^\circ$$

$$\text{power factor} = \cos 86.34^\circ = 0.0679$$

lag.

Q2(b)

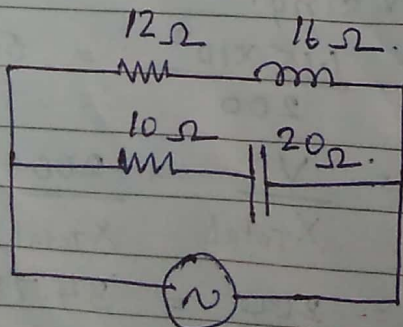

230V, 50 Hz  
1- $\phi$ , AC Supply

Branch 1  $\rightarrow 12 + j16 \Omega$

Branch 2  $\rightarrow 10 - j20 \Omega$

For Branch 1  $(12 + j16 \Omega \text{ Branch})$ .

$$I = \frac{V}{Z_1} = \frac{230 \angle 0^\circ}{12 + j16} = \frac{230 \angle 0^\circ}{20 \angle 53.3^\circ} = 11.5 \angle -53.3^\circ \text{ A.}$$

$$Z_1 = 20 \angle 53.3^\circ \Omega \quad \phi_1 = 53.33^\circ$$

$$\text{Active power} = P_1 = VI_1 \cos \phi_1 = 230 \times 11.5 \cos(-53.3^\circ) = 1580.7 \text{ W} = 1.580 \text{ kW}$$

$$\text{Reactive power} = Q_1 = VI_1 \sin \phi_1 = 230 \times 11.5 \sin(-53.3^\circ) = 2120.6 \text{ VAR} = 2.12 \text{ KVAR.}$$

$$\text{Apparant power} = VI_1 = 11.5 \times 230 = 2645 \text{ VA} = 2.645 \text{ KVA}$$

$$\text{power factor} = \cos(\phi_1) = \cos(-53.33) = 0.5972 \text{ lagging}$$

For Branch 2  $(10 - j20 \Omega)$ .

$$I_2 = \frac{V}{Z_2} = \frac{230}{10 - j20} = \frac{230}{22.36 \angle -63.43^\circ} = 10.28 \angle 63.43^\circ \text{ A.}$$

$$P_2 = VI_2 \cos(\phi_2) = 230 \times 10.28 \cos(63.43) = 1.057 \text{ kW}$$

$$Q_2 = VI_2 \sin(\phi_2) = 230 \times 10.28 \sin(63.43) = 2.114 \text{ KVAR.}$$

$$S_2 = VI_2 = 230 \times 10.28 = 2.364 \text{ KVA.}$$

$$\text{power factor} = \cos(\phi_2) = \cos(63.43) = 0.4472 \text{ leading}$$



Q.3 ✓ Attempt any one.

(a)  $L = 0.2 \text{ H}$

$R = 20 \Omega$

$C = 200 \mu\text{F}$

(i)

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$= \frac{1}{2\pi} \sqrt{\frac{1}{0.2 \times 200 \times 10^{-6}} - \left(\frac{20}{0.2}\right)^2}$$


$f_0 = 19.49 \text{ Hz}$  = Resonance frequency

(\*) Dynamic Impedance

$$Z_D = \frac{L}{CR} = \frac{0.2}{200 \times 10^{-6} \times 20} = 50 \Omega$$

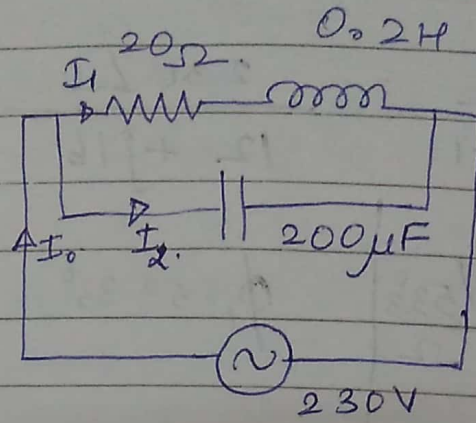(ii) Current

$$I = \frac{V}{Z_D} = \frac{230}{50} = 4.6 \text{ A}$$




$$\begin{aligned}
 Z_1 &= 20 + j2\pi fL \quad \Omega \\
 &= 20 + j2\pi \times 19.49 \times 0.2 \quad \Omega \\
 &= 20 + j24.49 \quad \Omega \\
 Z_1 &= 31.62 \angle 50.76^\circ \quad \Omega
 \end{aligned}$$

$$\begin{aligned}
 Z_2 &= -jX_C = \frac{-j}{2\pi fC} = \frac{-j}{2\pi \times 19.49 \times 200 \times 10^{-6}} \\
 Z_2 &= -j40.82 \quad \Omega = 40.82 \angle -90^\circ \quad \Omega
 \end{aligned}$$

$$\therefore I_1 = \frac{V}{Z_1} = \frac{230}{31.62 \angle 50.76^\circ} = 7.27 \angle -50.76^\circ \text{ A}$$

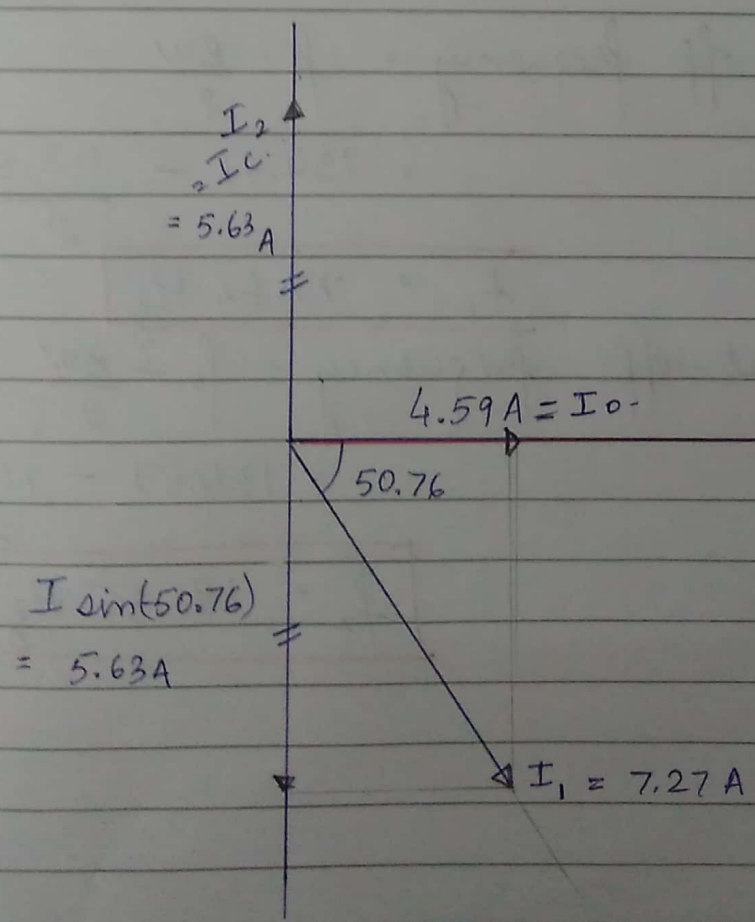
$$I_2 = \frac{V}{Z_2} = \frac{230}{40.82 \angle -90^\circ} = 5.634 \angle 90^\circ \text{ A}$$



phasor diagram.



Q.3(b) ✓ R-L-C series circuit

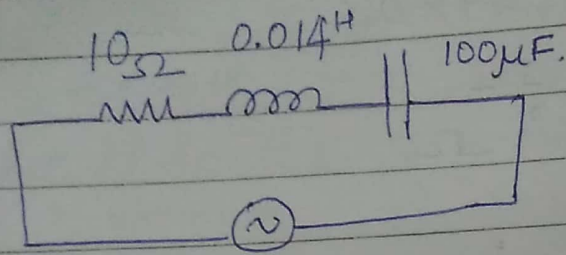

$$L = 0.014 \text{ H.}$$
$$C = 100 \mu\text{F}$$
$$R = 10 \Omega.$$

$$(i) \text{ Resonant frequency} = \frac{1}{2\pi\sqrt{LC}} = 134.51 \text{ Hz.}$$

$$(ii) \text{ Quality factor ; } Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.014}{100 \times 10^{-6}}} = 1.183$$

$$(iii) \text{ Band width} = \frac{R}{2\pi L} = \frac{10}{2\pi \times 0.014} = 113.68 \text{ Hz.}$$

$$(iv) \text{ lower cut-off frequency} = f_0 - \frac{BW}{2}$$
$$= 134.51 - \frac{113.68}{2}$$

$$f_1 = 77.66 \text{ Hz.}$$

$$(v) \text{ upper cut-off frequency} = f_0 + \frac{BW}{2}$$
$$= 134.51 + \frac{113.68}{2}$$

$$f_2 = 191.35 \text{ Hz.}$$